

00513

**B.Tech. ELECTRONICS
ENGINEERING - III
(BTCVI/BTECVI/BTELVI)**

Term-End Examination

December, 2012

**BIEE-001 : BASICS OF ELECTRICAL
ENGINEERING**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is allowed. All the questions are to be answered in English Language only.

1. (a) Explain star-delta transformation and vice-versa. 2x5=10
- (b) Find the voltage across $6\ \Omega$ resistor for the circuit shown in figure (1).

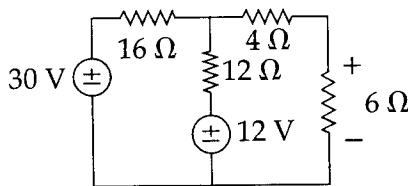


Figure (1)

2. (a) State and explain Thevenin's Theorem and write its limitations and applications. 2x5=10

- (b) Find the Norton equivalent circuit of the circuit shown in figure (2) at terminal a – b.

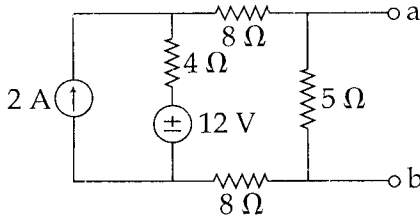


Figure - (2)

3. (a) What is the difference between primary and secondary cell ? **2x5=10**
(b) Explain the construction and working of silver oxide cell.
4. (a) Draw and explain hysteresis loop. What is its significance ? **2x5=10**
(b) Derive an expression for the force experienced by current carrying conductor placed in a uniform magnetic field.
5. (a) Explain the self inductance and mutual inductance. **2x5=10**
(b) State and explain Faraday's law of electromagnetic induction.
6. Show that the condition for resonance in a parallel R-L-C circuit is same as that in a series R-L-C circuit. State the application of series as well as parallel resonance. **10**

7. The following figure (3) shows a series - parallel circuit. Find : 10
- (a) Admittance of each parallel branch
- (b) Total circuit impedance
- (c) Supply current and power factor
- (d) Total power supplied by the source

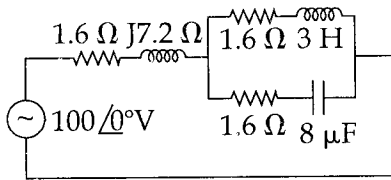


Fig. (3)

8. A balanced delta-connected load of impedance $(16 + j12) \Omega$ per phase is connected to a 3-phase 400 V supply. Find the phase current, line current, power factor, reactive power and total power. 10
9. Explain two wattmeter method to determine power in three-phase system. 10
10. Write short notes on *any two* of the following : $2 \times 5 = 10$
- (a) Superposition Theorem
- (b) Polyphase system
- (c) Difference between DC and AC.