

DECVI/DELVI/DCSVI/ACECVI/ACELVI/
ACSVI

Term-End Examination

December, 2012

BIEL-027 : APPLIED ELECTRONICS

Time : 2 Hours

Maximum Marks : 70

- Note :
- (1) Question No. 1 is *compulsory*.
 - (2) Attempt *any five* questions.
 - (3) Each question carry *equal* marks.
 - (4) Use of scientific calculator is *allow*.
 - (5) Answer must be given in English only.

1. This question contains fill in the blanks type questions. 7x2=14
- (a) Frequency distortion in an amplifier is caused by _____ .
 - (b) The maximum theoretical collector circuit efficiency of transformer coupled class - A amplifier is _____ .
 - (c) A transistor amplifier with collector circuit efficiency of 15% is likely to be _____ .
 - (d) Full form of MOSFET is _____ .
 - (e) A bistable multivibrator has _____ .
 - (f) In a multivibrator, commutating capacitor reduce the _____ .
 - (g) Bootstrap voltage sweep generator uses _____ .

2. (a) Draw the circuit of CS amplifier. Draw and explain the frequency response of CS amplifier. 7
- (b) Draw the circuit diagram of class B push pull amplifier and explain its working and concept of cross over distortion. 7
3. (a) What is Barkhausen Criterion for oscillation ? What disadvantage does a phase shift oscillator have ? How is this removed in a Wien bridge oscillator ? 7
- (b) Draw a Colpitts oscillator circuit. Explain how the stable oscillations are obtained. Derive the expression for the frequency obtained. 7
4. (a) What is a UJT ? Explain its principle of construction. Give its application. 7
- (b) Explain the effect of negative feedback on : 7
- (i) frequency distortion
- (ii) reduction of noise.
5. (a) What is the need for trouble shooting ? Explain the important steps for testing. 7
- (b) Derive the o/p resistance and i/p resistance of voltage series feedback amplifier. 7

6. (a) Draw and explain the working of BMV. 7
Give its specific application.
- (b) Obtain the co-ordinates of Q point for the self bias circuit shown in figure (1) 7

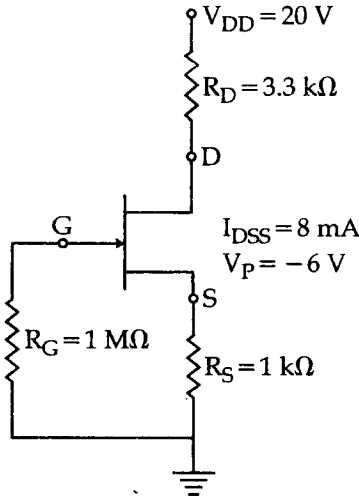


Figure - (1)

7. (a) Find the output voltage for the network of figure - 2 for the input indicated in same figure. 7

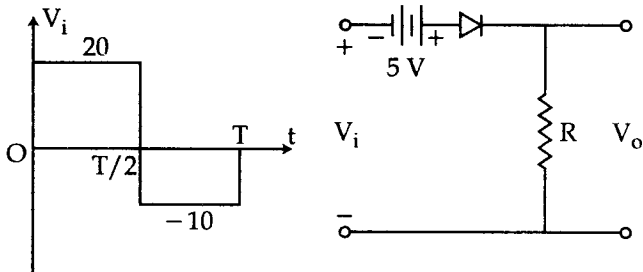


Figure - (2)

- (b) Determine V_0 for the network of figure -3 for the i/p indicated in same figure. 7

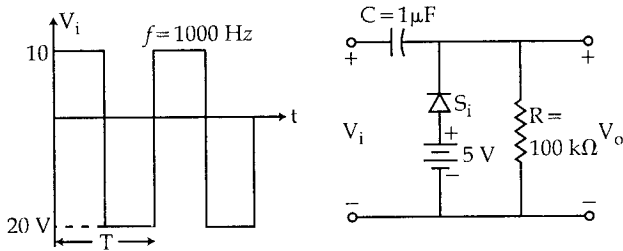


Figure - (3)

8. Write short notes on *any four* of the followings. 4×3.5=14
- Crystal oscillator.
 - Bootstrap sweep generator.
 - Tuned amplifier.
 - Depletion Type MOSFET.
 - Trouble shooting of phase shift oscillator.
 - Heat Sink.