

00771

DECVI

Term-End Examination

December, 2012

BIEL-038 : LINEAR INTEGRATED CIRCUITS

Time : 2 hours

Maximum Marks : 70


-
- Note : 1. First question is *compulsory* and attempt *any four* from rest.
2. Use of scientific calculator is *permitted*.
-

1. (a) An OP-AMP comparator circuit employs : 2x7=14
- (i) No feedback
 - (ii) Positive feedback
 - (iii) Negative feedback
 - (iv) Any type of feedback
- (b) The closed loop gain of an OP-AMP inverting amplifier is :
- (i) Larger than unity
 - (ii) Less than unity
 - (iii) Equal to unity
 - (iv) Anything

- (c) Duty cycle of astable MV for $R_A = 5 \text{ k}\Omega$
 $R_B = 10 \text{ k}\Omega$ and $C = 0.05 \text{ }\mu\text{F}$.
- (i) 0.5 (ii) 0.2
 (iii) 0.6 (iv) 0.75
- (d) Slew rate of an ideal OP-AMP is :
- (i) Zero (ii) Infinite
 (iii) $1 \text{ V}/\mu\text{s}$ (iv) $5 \text{ V}/\mu\text{s}$
- (e) Butter worth polynomial of order 'n' has magnitude _____.
- (f) The output impedance of an active filter is :
- (i) In range from a fraction of an ohm to a few hundred ohms.
 (ii) Infinite
 (iii) Several $\text{K}\Omega$
 (iv) Several $\text{M}\Omega$
- (g) In a switched-capacitor filter, the electronics switches are :
- (i) MOSFET (ii) BJT
 (iii) Diode (iv) Capacitor

2. (a) State the characteristics of ideal and practical OP-AMP. **6**
- (b) Derive the expressions for the voltage gain and input impedance of an inverting amplifier using OP-AMP. **8**

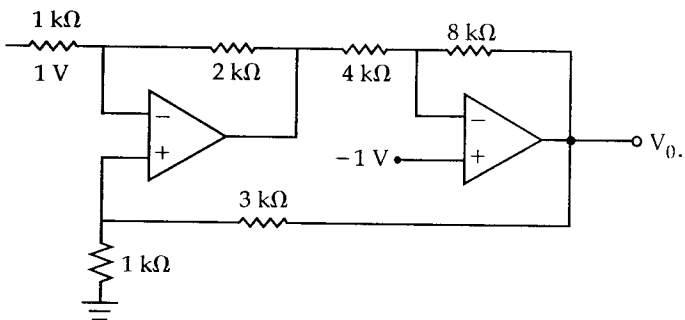3. (a) What type of feedback is used in an OP-AMP adder ? Justify your answer. 6
 (b) Draw the circuits of voltage to current and current to voltage convertors using OP-AMP. 8
4. (a) Discuss the effect of slew rate on bandwidth and output impedance. 6
 (b) Draw neat diagram of first order HP Butter worth filter. Derive the equation for the gain of filter. 8
5. (a) Write the advantages of active filter over passive filter. 6
 (b) Explain the operation of a switched capacitor filter. List out the advantages of a switched capacitor filter. 8
6. (a) Draw the pin diagram of IC 555. Explain the functions of different pins of IC 555. 6
 (b) Draw the diagram of bistable MV and explain the operation with the help of output waveform. 8
7. (a) Find the output voltage V_0 for given circuit. 8



- (b) Design a first order Butterworth active HP filter having a cut off frequency of 200 Hz and high frequency gain of 5. 6

8. Attempt *any four* of followings : 3.5x4=14

- (a) Slew rate and CMRR of OP-AMP
 - (b) Process of offset nulling in OP-AMP
 - (c) Concept of virtual grounding in OP-AMP
 - (d) Frequency response of band pass and band reject filter
 - (e) Notch filter
 - (f) Different modes of IC Timer 555
-