

00543

**B.Tech. ELECTRONICS AND
COMMUNICATION**

Term-End Examination

December, 2012

BIELE-004 : RF CIRCUITS

Time : 3 hours

Maximum Marks : 70

*Note : Attempt **any seven** questions. Assume the missing data, if any.*

1. Describe the characteristics of following components at radio frequencies (take the proper assumptions as needed). **5x2=10**
 - (a) Capacitors
 - (b) Inductors

2. Derive the expression for input Impedance of a transmission line. **10**

3. Discuss the model for active components at radio - frequencies. **10**

4. (a) Describe briefly shunt amplifier. Also give relevant expressions. **5x2=10**
(b) What do you mean by neutralization ? Explain with relevant expression.

5. (a) Discuss about LNA topologies in brief. $5 \times 2 = 10$
(b) Analyze LNA for large signal performance.
 6. (a) Describe the characteristics of Ideal mixers.
(b) Compare the performance of Diode - Ring mixer with other common mixer. $5 \times 2 = 10$
 7. Discuss the working principle of class AB Power amplifier with suitable circuit diagrams. 10
 8. How the modulation of power amplifiers is done ? 10
Describe in detail.
 9. What are the negative resistance oscillators ? 10
Describe their working in detail.
 10. Describe RF synthesizer with dithering moduli in detail. 10
-