No. of Printed Pages: 3

ET-202(B)

B.Tech. Civil (Construction Management)/ B.Tech. Civil (Water Resources Engineering)

00381 Term-End Examination
December, 2014

ET-202(B): PRINCIPLES OF ELECTRICAL SCIENCES

Time: 3 hours

Maximum Marks: 70

Note: Answer any **five** questions. Symbols and abbreviations have their usual meaning. Use of calculator is permitted.

- 1. (a) State and explain Maximum power transfer theorem.
 - (b) Explain the different types of dependent sources.
- **2.** (a) Explain the term active power, apparent power and power factor. How is the power factor corrected?
 - (b) A voltage $200\sqrt{2}$ sin (314t+60) is applied across a load comprising $R=60\,\Omega$ and $L=200\,\text{mH}$ in series. Find the power drawn by the load and its power factor.

8

6

7

3.	(a)	Write short notes on any two of the following: 2×3	:=6
		(i) Difference between power transforme and instrument transformer	r
		(ii) Errors in measurement(iii) Range and extension of moving iron	
	(b)	ammeter and voltmeter Explain the basic features of an analog indicating instrument. What is the need of damping torque in an analog indicating instrument?	8
4.	(a)	Explain different types of D.C. machines and derive its e.m.f. equation.	7
•	(b)	Explain slip torque characteristics of 3-phase induction motor.	7
5.	(a)	What are the advantages and disadvantages of MOSFET over BJT? Describe the operation of MOSFET and its characteristics with suitable diagram.	7
	(b)	_	7
6.	(a)	Write the disadvantages of RC Phase shift oscillator. Draw the circuit diagram of RC Phase shift oscillator. Derive the expression for frequency.	7
	(b)	Explain the basic principle of C.R.O. and give its applications.	7

7.	(a)	Explain the addressing modes of 8085 with the help of an example.	7
	(b)	What is micro-processor? Draw the architecture of micro-processor and differentiate between micro-processor and CPU.	7
8.	(a)	Write short notes on any two of the following: $2 \times 3 \frac{1}{2} =$	7
		(i) Digital to Analog Converter	
		(ii) Digital Counter	
		(iii) Multiplexer	

Explain the successive approximation type

Analog to Digital Converter.

(b)