

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

00290

December, 2014

**BIEL-003 : DIGITAL ELECTRONICS**

*Time : 3 hours**Maximum Marks : 70*


---

*Note : Attempt any **seven** questions. All questions carry equal marks.*

---

1. (a) Using 4 variable K map, find all the prime implicants of the following function : 6  
 $f(w, x, y, z) = \sum (0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$ .
- (b) Determine the binary numbers represented by the following decimal numbers : 4
- (i) 0.6875
- (ii) 25.5
2. (a) Prove the following equations using the Boolean algebraic theorems : 8
- (i)  $A + \bar{A} \cdot B + A \cdot \bar{B} = A + B$
- (ii)  $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + BC + AC$
- (b) Verify that the NAND operation is commutative. 2


3. Discuss in detail, the working of Full Adder logic circuit and extend your discussion to explain a binary adder, which can be used to add two binary numbers (each having four bits). 10

4. (a) What is a digital comparator ? Explain the working of a 2-bit digital comparator with the help of truth table. 5

(b) What is a decoder ? Draw the logic circuit of a 3-line to 8-line decoder and explain its working briefly. 5

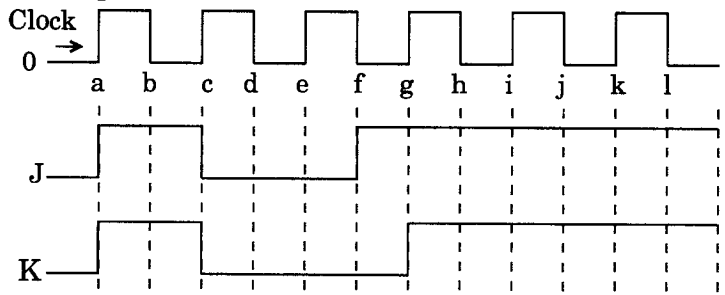5. What is a flip-flop ? Write the truth table for a clocked J-K flip-flop which is triggered by the positive edge of the clock signal. Explain the operation of this flip-flop for the following conditions :

Initially all inputs are zero and assume the 'Q' output to be 1. 10



6. (a) Using D-flip-flops and waveforms explain the working of a 4-bit SISO shift register. 6

(b) Distinguish between combinational logic circuits and sequential logic circuits. 4

7. (a) Give the circuit of a TTL NAND gate and explain its operation in brief. 6
- (b) Explain the following characteristics for digital ICs : 4
- (i) Propagation delay
- (ii) Power dissipation
8. (a) Describe CMOS inverter and state the advantages of CMOS. 6
- (b) Mention the various IC logic families. 4
9. Differentiate between static and dynamic RAM. Draw the circuits of one cell of each and explain its working. 10
10. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Concept of PLA
- (b) Pseudo Random Binary sequencing generator
- (c) Design of ALU
-