

**DIPLOMA – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

Term-End Examination

00455

December, 2014

BIEL-038 : LINEAR INTEGRATED CIRCUITS

Time : 2 hours

Maximum Marks : 70

Note : *First question is compulsory and attempt any four from the rest. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, should be assumed.*

1. (a) What is used to eliminate the effect of offset voltage ?
- (i) Voltage offset null circuit
 - (ii) Resistor feedback
 - (iii) Feedback circuit with passive device
 - (iv) None of the above
- (b) The op-amp integrator and differentiator are useful for
- (i) clipping circuit
 - (ii) wave-shaping circuit
 - (iii) clamping circuit
 - (iv) None of the above

- (c) The application of PLL is
- (i) Charging device
 - (ii) Wave generator
 - (iii) AM and FM demodulator
 - (iv) All of the above
- (d) The voltage gain of a basic instrumentation amplifier is set by
- (i) Diode
 - (ii) Capacitor
 - (iii) Resistor
 - (iv) Inductor
- (e) The Duty cycle of astable operation using IC-555 is
- (i) $\frac{R_A + R_B}{2 (R_A + R_B)}$
 - (ii) $\frac{2 R_A + R_B}{R_A + R_B}$
 - (iii) $\frac{R_A + R_B}{2 R_A + R_B}$
 - (iv) $\frac{R_A + R_B}{R_A + 2 R_B}$

(f) The critical frequency is defined as the point at which the response drops _____ from the pass band.

(i) - 20 dB

(ii) - 3 dB

(iii) - 6 dB

(iv) - 40 dB

(g) An op-amp as a voltage follower has a voltage gain of

(i) Infinity

(ii) Zero

(iii) Unity

(iv) Less than unity

$7 \times 2 = 14$

2. (a) Why is differential amplifier used as an input stage of op-amp ? Draw and explain the circuit diagram of push-pull amplifier used in output stage of an op-amp. 8

(b) Define the following parameters as applied to an op-amp : $2+2+2=6$

(i) SVRR

(ii) CMRR

(iii) Output voltage swing

3. (a) Draw the circuit diagram of an op-amp based practical differentiator and derive an expression for the output in terms of the input. What are the disadvantages of an ideal differentiator? 2+4+2=8
- (b) For a non-inverting amplifier shown in figure 1, calculate (i) A_{CL} (ii) V_o (iii) I_L . 6

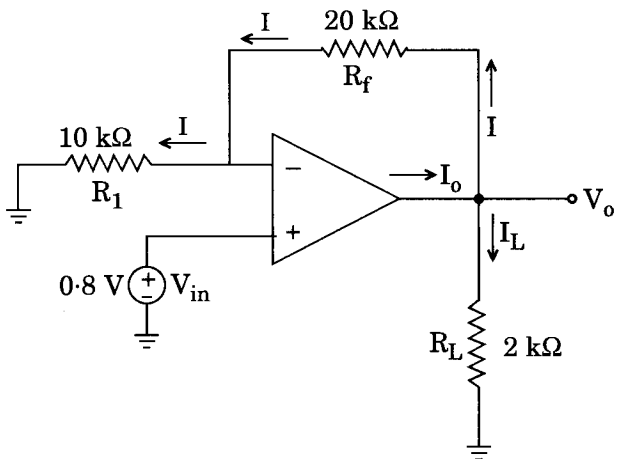


Figure 1

4. (a) With the help of neat diagram and waveform explain the Schmitt trigger. Write down the comparison between Schmitt trigger and Comparator. 4+4=8
- (b) Draw and explain the circuit diagram of sample and hold circuit with necessary waveform and expressions. 6

5. (a) Explain the operation of second order low pass Butterworth filter with their frequency response. 8
- (b) Explain with neat diagram, the operation of wide-band pass filter. What is roll-off rate for a third order low pass filter? 6
6. (a) Draw the circuit diagram of an astable multivibrator to generate the output signal with frequency of 1 KHz and the duty cycle of 75%. Consider the value of capacitor in the circuit diagram is $0.1 \mu\text{F}$. 8
- (b) Explain the use of IC-555 as a monostable multivibrator with necessary diagrams and waveforms. 6
7. (a) A 555 timer is configured to run in astable mode with $R_A = 4 \text{ k}\Omega$, $R_B = 4 \text{ k}\Omega$ and $C = 0.01 \mu\text{F}$. Determine the frequency of the output and duty cycle. Define duty cycle. 8
- (b) Draw and explain the transfer characteristics of PLL. 6

8. (a) Explain the working of PLL using appropriate block diagram. Derive the expression for capture range of PLL IC-565.

4+4=8

(b) Explain how 565 PLL IC can be used as a FSK demodulator with necessary diagram. 6
