

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**December, 2017**

00559

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS  
DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

---


*Note : Attempt any **seven** questions. All questions carry equal marks. Missing data may be suitably assumed and mentioned. Use of scientific calculator is permitted.*

---

---

1. (a) Write the characteristics of an ideal op-amp. 5
- (b) Why are differential amplifiers preferred over single-ended amplifiers ? Explain. 5
2. (a) Derive the expressions of closed loop gain in both, inverting and non-inverting configurations. 5
- (b) Discuss the various Grounding and Shielding techniques. 5

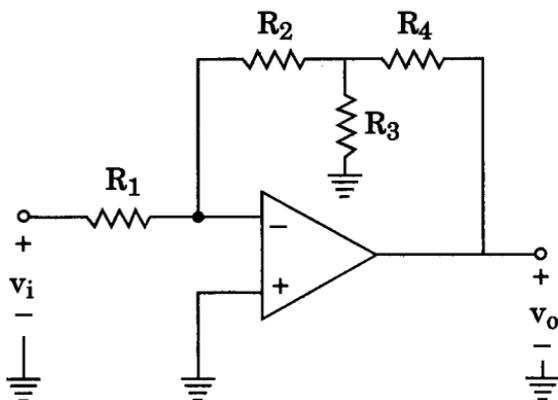3. (a) Assuming the op-amp to be ideal, derive an expression for the closed-loop gain  $v_o/v_i$  of the circuit as shown below.



Use this circuit to design an inverting amplifier with a gain of 100 and an input resistance of 1 M $\Omega$ . Assume that for practical reasons it is required not to use resistors greater than 1 M $\Omega$ .

5

- (b) Draw the voltage follower circuit using op-amp, and show that the gain is unity. Draw its equivalent circuit model.

5

4. (a) Draw the circuit diagram of the instrumentation amplifier using op-amp, and explain its operation principle by deriving the expression of gain.


5

- (b) Design a circuit using op-amp to get the output voltage  $v_o = 6v_1 + 4v_2$ .

5

5. (a) For the circuit as shown below, find the values of  $i_1$ ,  $i_I$ ,  $v_1$ ,  $i_2$ ,  $v_o$ ,  $i_L$  and  $i_o$ . Also find the voltage gain  $v_o/v_I$ , the current gain  $i_L/i_I$  and the power gain  $P_L/P_I$ .

8

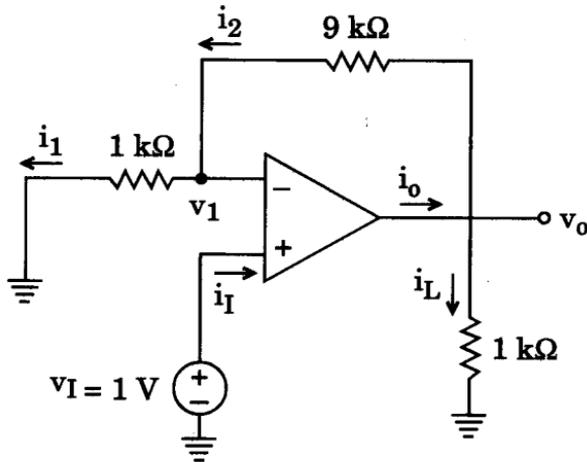

- (b) Define Common Mode Rejection Ratio of op-amp.

2

6. (a) Design a differentiator circuit using op-amp. Also derive its transfer function.

5

- (b) Explain the practical considerations of a differentiator circuit and its limitations.

5

7. (a) Design a Sample and Hold Circuit using op-amp. Explain its operation principle.

5

- (b) Design a Clipper Circuit and Clamper Circuit using op-amp.

5

8. (a) Design a circuit for generation of sawtooth waves using op-amp. 5
- (b) Design an op-amp based multivibrator circuit and explain its operation. 5
9. (a) What is the difference between Difference Amplifier and Comparator Circuit ? What are the limitations of op-amp as a comparator ? 5
- (b) Classify the types of Filters. Draw the circuit diagram of a 2<sup>nd</sup> order Sallen-key low pass filter. 5
10. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Log/Antilog Amplifier
- (b) Voltage Controlled Oscillator (VCO)
- (c) Phase Locked Loop (PLL) as FM Demodulator
-