

**BACHELOR OF TECHNOLOGY IN
MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING)**

Term-End Examination

June, 2008

**BME-021 : PRINCIPLES OF ELECTRICAL
AND ELECTRONICS SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Answer seven questions in all. Question number 1 is **compulsory**. Attempt any **three** questions from Section A and any **three** questions from Section B. All symbols and abbreviations used have their usual meanings.

1. State whether the following assertions are true or false :

10×1=10

- (i) Zener diode is used to regulate the load voltage.
- (ii) The emitter of transistor is doped lightly.
- (iii) Monostable multivibrator has more than one state.
- (iv) $\overline{A + B} = \overline{A} \overline{B}$ is the DeMorgan's theorem.


- (v) Active power in a 3 phase balanced circuit is $3 V_p I_p$.
- (vi) Frequency of the emf produced in the armature of an alternator is directly proportional to the speed of the rotor.
- (vii) The power factor of pure inductance is zero.
- (viii) Accumulator of 8085 microprocessor unit is a part of the Arithmetic Logic Unit (ALU).
- (ix) The voltage gain of an opamp can be changed easily by changing the ratio between values of the input and feedback resistors.
- (x) Kirchhoff's laws are applicable to DC circuits only.

SECTION 'A'

Answer any **three** of the following.

2. (a) Distinguish between self-inductance and mutual inductance. 4
- (b) A coil is wound uniformly with 400 turns over a steel ring of relative permeability 800, having a mean circumference of 40 mm and cross-sectional area of 50 mm^2 . If a current of 25 A is passed through the coil, find (a) mmf, (b) reluctance of the ring, and (c) flux. 6
3. (a) Define apparent power and reactive power of an A.C. circuit. 4
- (b) An inductive coil of resistance 32Ω and reactance 15.7Ω is connected in series with a capacitor of reactance 79.5Ω . The circuit is connected across 500 V A.C. supply. Determine
- (i) Current
 - (ii) Phase difference between voltage and current
 - (iii) Total power absorbed 6
4. (a) A three-phase, six pole induction motor is supplied from a 50 Hz, 400 V supply. Calculate the speed of the rotor when the slip is 3%. 4
- (b) Write the working principle of a three-phase induction motor. What are the main applications of single phase induction motors? 6

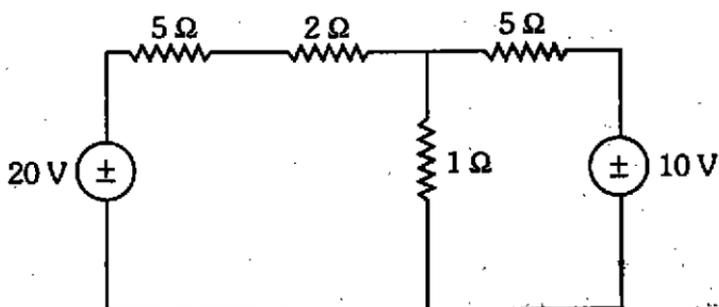5. (a) Explain series resonance in RLC series circuit. 4
(b) What are the most common materials used in the electrical and electronics devices ? Explain their properties and applications. 6
6. (a) State and explain Thevenin's theorem. 4
(b) Find the current passing through $2\ \Omega$ resistance by using Maxwell loop method. 6



SECTION 'B'

Answer any **three** of the following.

7. Draw the symbol, structure and equivalent circuit of SCR. List the applications of semiconductor diodes and transistors. 10
8. What are the various registers in 8085 ? Name the 16 bit registers. Also give the name of 5 different addressing modes. 10
9. Explain about Read Only Memory (ROM) and Random Access Memory (RAM) in detail. 10
10. State and explain De Morgan's Theorem. Verify that $A + BC = (A + B)(A + C)$. 10
11. What are the characteristics of ideal and practical operational amplifiers ? Draw the basic analog circuit for non-inverting amplifier. 10

