

**B.TECH. IN ELECTRONICS AND  
COMMUNICATION ENGINEERING (BTECVI)**

**Term-End Examination**

**December, 2013**

**BIELE-013 : DEVICE MODELLING FOR CIRCUIT  
SIMULATION**

*Time : 3 hours*

*Maximum Marks : 70*


*Note : Attempt any seven questions. All questions carry equal marks.*

1. A symmetrical  $p^+ - n - p^+$  bipolar transistor has the following properties : 10

$A = 10^{-4} \text{ cm}^2$	$\frac{\text{emitter}}{N_a = 10^{17}}$	$\frac{\text{base}}{N_d = 10^{15} \text{ cm}^{-3}}$
$W_b = 1 \text{ } \mu\text{m}$	$\tau_n = 0.1 \text{ } \mu\text{s}$	$\tau_p = 10 \text{ } \mu\text{s}$
$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$	$\mu_p = 200$	$\mu_n = 1300$
	$\mu_n = 700$	$\mu_p = 450$

- (a) Calculate the saturation current  $I_{ES} = I_{CS}$
- (b) With  $V_{EB} = 0.3\text{V}$  and  $V_{CB} = -40\text{V}$ , calculate the base current  $I_B$ , assuming perfect emitter injection efficiency.
- (c) Calculate the base transport factor  $B$ , emitter injection efficiency  $\gamma$  and amplification factor  $\beta$ , assuming that the emitter region is long compared with  $L_n$ .

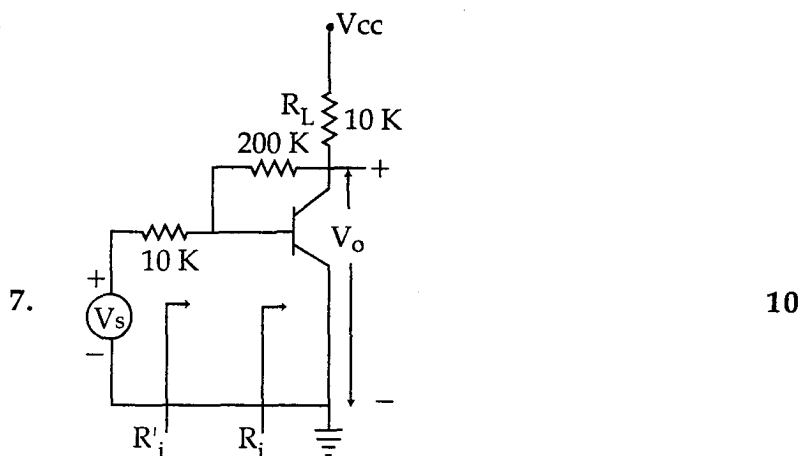2. Discuss the principle of circuit simulation with its objectives in detail. 10
3. (a) How a circuit is described in SPICE ? 5  
 (b) Define the BSIM model for MOS. 5
4. How the circuit elements can be modeled in SPICE ? Explain General format for model statement, also state the command for operating temperature, Independent dc sources and dependent sources. 10
5. Explain mobility model for MOSFET. Also explain short channel MOSFET I-V characteristics. 10
6. Write short note on : 5+5  
 (a) DIBL (Drain-induced Barrier lowering)  
 (b) MOS Capacitor



For the amplifier shown in above fig. Calculate

$$R_i, R_i', A_v, A_{v_s} \text{ and } A_I' = \frac{-I_2}{I_1}$$

[Given  $h_{fe} = 50$ ,  $h_{oe} = \frac{1}{40} \Omega$ ,  $h_{ie} = 1.1K$ ,  
 $h_{re} = -250 \times 10^{-6}$  ]

8. (a) Draw and explain the small signal equivalent circuit for an emitter-follower stage at high frequencies. 5
- (b) Explain, why the 3-dB frequency for current gain is not the same as  $f_H$  and for voltage gain? 5
9. (a) Define  $f_\beta$  and  $f_\tau$  and what is the relationship between  $f_\beta$  and  $f_\tau$ . 5
- (b) Derive the expression for the CE short circuit current gain  $A_i$  as a function of frequency. 5
10. Explain short and narrow channel MOSFETs with suitable diagram. What is the difference between JFET and MESFET modelling? 6+4
-