

B.TECH.-ELECTRICAL ENGINEERING**Term-End Examination****December, 2013****BIEE-017 : DIGITAL ELECTRONICS***Time : 3 hours**Maximum Marks : 70*

Note : Attempt *any seven* questions as the following.*Assume the missing data if any.*

1. Derive the Boolean expression for a two input Ex-NOR gate to realize with two input NOR gates, without using complemented variables and draw the circuit. 10
2. Expand the Boolean expression $A(\bar{A} + B)$ $(\bar{A} + B + \bar{C})$ to mini terms. 10
3. Reduce the expression $f = \text{TTM} (0, 1, 2, 3, 4, 7)$ using K - map and implement it in NOR logic. 10
4. What is full subtractor ? Design a full subtractor and discuss with an example. 10
5. Implement the logic function : $F = A \oplus B \oplus C$, using a 8×1 MUX 10
6. What are flip-flops ? Explain the working of S-R flip flop in detail. 10

7. What is race around condition in flip-flop ? 10
Discuss the method to overcome the race around condition.
8. Why 8085 microprocessor is called 8 bit 10
microprocessor ? Explain the working of 8085 with a neat diagram.
9. What are different addressing modes used in 8086 10
microprocessor ? Explain with examples.
10. Write the short notes on **any two** of the following : 5x2=10
- (a) BCD Adder
 - (b) Counterx
 - (c) Segment override prefix
-