

DIPLOMA IN ECE ENGINEERING

Term-End Examination

December, 2013

BIELE-006 : ELECTRONIC PRODUCT DESIGN

Time : 2 hours

Maximum Marks : 70

*Note : (i) Attempt **any five** questions in all.*

*(ii) Question no. 1 is **compulsory**.*

-
1. (a) Mention specifications of regulated power supply. 7x2=14
 - (b) Which material is used for fuse and why?
 - (c) Comment on MSI and LSI devices.
 - (d) Give a comparison of FSM and ASM.
 - (e) List the merits of analog filter design over digital filter design.
 - (f) Compare transducer and sensor.
 - (g) Describe analog signal conditioning circuit.

 2. (a) Explain regulated dc power supply with the help of circuit diagram and also explain various types of filters used for dc power supply. 7
 - (b) Explain the functions of EMI filters and MCB. 7

3. Analyze the synchronous circuit given in figure-1 and 14
- (a) Write excitation and output function.
- (b) Form the excitation and state table.
- (c) Give word description of the circuit.

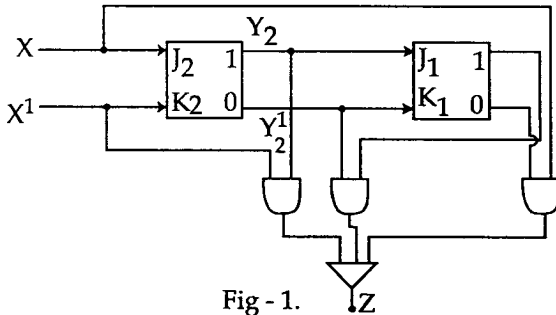


Fig - 1.

4. (a) Implement the following function using 8 to 1 Mux : $F(x,y,z) = \sum m(0,2,3,5)$. 7
- (b) Explain Moore and Mealy machines, with state diagrams in detail. 7
5. Explain various realization techniques of all-pass and KRC filters. 14
6. (a) Design a third order 0.1dB chebyshev high pass filter with $f_c = 100\text{Hz}$ and high frequency gain $H_0 = 20\text{dB}$. 7
- (b) Derive the formulas for transfer functions of band pass and band stop filters. 7

7. Explain the procedure to select a transducer and A/D converter for data acquisition system for assumed specifications, with suitable example. **14**
8. Write short note on **any four** : **$3\frac{1}{2} \times 4 = 14$**
- (a) Circuit design verification using simulation software.
 - (b) Combinational design using PLD's.
 - (c) Sensitivity analysis.
 - (d) Cascading of filters.
 - (e) DAC Interfacing.
 - (f) Selection of Microcontroller.
-