

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

00119

December, 2014

BIEL-019 : POWER ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **five** questions in all. All questions carry equal marks. Missing data if any may be suitably assumed. Use of scientific calculator is permitted.

1. (a) Explain the different methods of turning on of an SCR. 7
- (b) Explain the principle of operation of the IGBT and its advantages over the power transistor. 7
2. (a) Discuss the working of a single-phase series inverter. What are the limitations of a series inverter ? 7
- (b) Explain how regenerative braking can be achieved by means of a dual converter bridge. 7
3. (a) What are the techniques used to control the operation of a chopper circuit ? 7

- (b) A 60 V battery supplies an inductive load through a chopper circuit. The load inductance and resistance are 30 mH and 5 Ω respectively. The load has a freewheeling diode across it. What should be the time ratio and duty cycle of the chopper, if average output voltage of the chopper is 45 V ? 7
4. (a) With the help of a circuit and waveforms diagrams, describe the working principle of three-phase full controlled rectifier. 7
- (b) Explain the working of modified McMurray half bridge inverter with the help of a neat diagram. 7
5. Explain how the speed of a dc series motor can be controlled by using thyristors (SCRs). What are the parameters to be varied for speed control of a separately excited dc motor ? 14
6. (a) Define the following : 8
- (i) Latching current
- (ii) Holding current
- (iii) Commutation
- (iv) Firing
- (b) Explain the speed control of induction motor by Stator Voltage Control method. 6
7. Write short notes on any **two** of the following : $2 \times 7 = 14$
- (a) GTO
- (b) Current Source Inverter
- (c) Slip Power Recovery Scheme