

**B.Tech. – VIEP – ELECTRICAL ENGINEERING  
(BTELVI)**

00205

**Term-End Examination**

**December, 2014**


**BIEE-014 : NETWORK THEORY**

*Time : 3 hours*

*Maximum Marks : 70*

**Note :** Attempt any **five** questions. All questions carry equal marks.

1. (a) Distinguish between 7
- (i) tree and co-tree
  - (ii) mesh and loop
  - (iii) planar and non-planar graph
  - (iv) incidence matrix and reduced incidence matrix
- (b) Draw the graph of the network shown in the Fig. 1. Select a suitable tree to write tie-set schedule. Hence find the three loop currents. 7

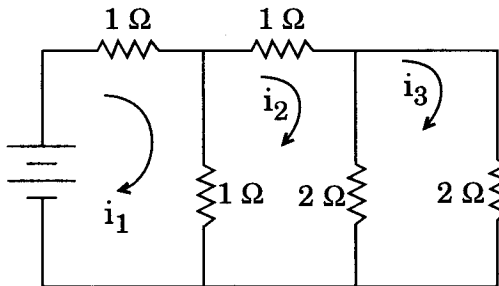

*Fig. 1*

2. (a) (i) Explain maximum power transfer theorem for ac circuit.
- (ii) In the network shown in Fig. 2 two voltage sources act on the load  $Z_L$ . If the load is variable, for what value load  $Z_L$  will receive maximum power ?

7

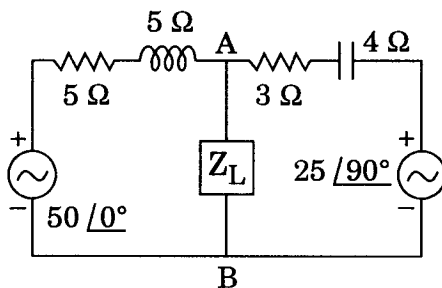


Fig. 2

- (b) State and prove Millman's Theorem.
3. (a) What is driving point impedance ? Determine the driving point impedance  $Z_{11}(s)$  of the network shown in the Fig. 3.

7

7

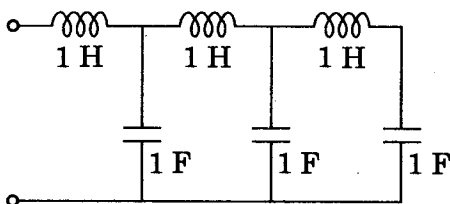


Fig. 3

- (b) What are poles and zeroes ? Explain the significance of the poles and zeroes in the network functions.

7

4. (a) (i) Derive the condition of reciprocity for Z-parameters.

(ii) Check whether the network shown in the Fig. 4 is reciprocal or not.

7

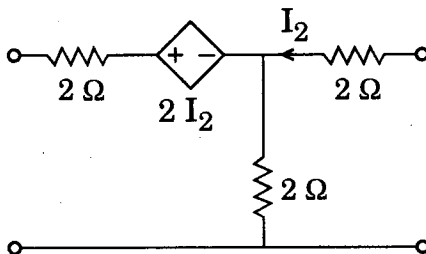


Fig. 4

(b) Why are ABCD parameters known as transmission parameters ? Two identical sections of the network shown in the Fig. 5 are cascaded. Calculate the transmission parameters of the resulting network.

7

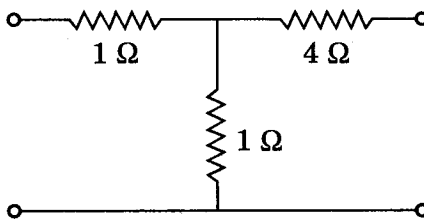


Fig. 5

5. (a) (i) State clearly the conditions to be fulfilled for a function to be positive real.

(ii) Justify  $F(s) = s + \sqrt{s^2 + 1}$  is a positive real function.

7

- (b) Realise the following RC driving point impedance function in Foster-I form

$$Z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s} \quad 7$$

6. (a) The image impedances of the network shown in the Fig. 6 are  $Z_{i1} = 100 \Omega$  and  $Z_{i2} = 50 \Omega$ . Calculate the values of impedances  $Z_1$  and  $Z_2$ . 7

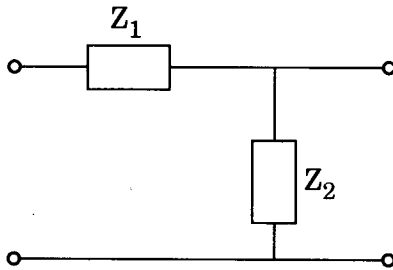


Fig. 6

- (b) What is high pass filter ? Prove the cut-off frequency  $f_c = \frac{1}{4\pi\sqrt{LC}}$  for constant-K high pass filter (T-section). 7
7. Write short notes on any **two** of the following :  $2 \times 7 = 14$
- (a) Compensation Theorem
  - (b) Transfer function and its properties
  - (c) Interconnections of two port networks
  - (d) Procedure for testing positive real functions