

**BACHELOR OF TECHNOLOGY IN
MECHANICAL ENGINEERING (COMPUTER
INTEGRATED MANUFACTURING) /
B.Tech. (AEROSPACE ENGINEERING) (BTAE)**

Term-End Examination

01175

December, 2014

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Answer any seven questions in all — three question from section A, three questions from section B. Question one is compulsory.

1. State whether the following statements are *True* or *False*. *10 × 1 = 10*

- (a) In short circuit test, the iron losses are negligible.
- (b) A three-phase induction motor has zero torque at synchronous speed.
- (c) In delta connected systems, the reactive power is given by the relation,


$$\sqrt{3} V_{Ph} I_{Ph} \cos \phi$$

- (d) The RLC series circuit is inductive at resonance.
- (e) Sine wave has unity form factor.
- (f) TRAP hardware interrupt has the highest priority.
- (g) 80386 Microprocessor is code-named as P3.
- (h) Universal motor is a constant speed motor.
- (i) TRIAC can conduct in both directions.
- (j) AND gate is a universal gate.


SECTION A

Attempt **three** questions from this section.

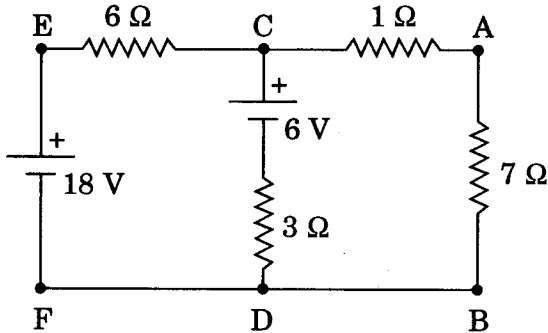2. (a) State and explain Norton's theorem with suitable example. 4
- (b) Using Thevenin's Theorem, calculate the potential difference across terminal A and B, as shown in Figure 1.



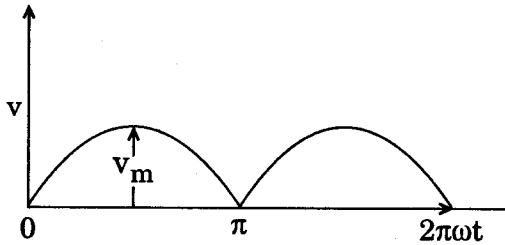3. (a) For the output of full wave rectifier, determine 6
- (i) rms value
 - (ii) average value
 - (iii) form factor



- (b) Explain series resonance. Why is series resonance called voltage resonance? 4

4. (a) What is coefficient of coupling ? Prove that $K = \frac{M}{\sqrt{L_1 L_2}}$, where K, M, L_1 , L_2 have their usual meanings. 6
- (b) What is magnetic circuit ? Explain B-H curve as applied to magnetic material. 4
5. (a) Why is single phase induction motor not self-starting ? Explain. 4
- (b) What is a transformer ? Explain its principle of working. 3
- (c) A three-phase 4-pole, 50 Hz induction motor is rotating at 1450 rpm. Find out synchronous speed and % slip of induction motor. 3
6. (a) Prove that the energy stored in an inductor is given by $\frac{1}{2} LI^2$. 4
- (b) A coil of 100 turns is wound on toroidal magnetic core having reluctance of 10^4 At/Wb. When the coil current is 5 A, and is increasing at the rate of 200 A/sec, determine
- (i) self-inductance of coil,
 - (ii) energy stored
 - (iii) self-induced emf in coil.

SECTION B

Attempt **three** questions from this section.

7. (a) Explain the data bus, address bus and control bus in a typical microprocessor architecture. Give a suitable diagram. Explain the architecture. 6
- (b) Explain the various registers of 8085. Name the 16-bit registers. Discuss the role of each register in mathematical operations. 4
8. (a) Explain the operation of a Negative-Impedance Converter (NIC) using op-amp. 5
- (b) Draw the small signal equivalent circuit of BJT and MOSFET. 5
9. (a) Draw the block diagram of IC 555 timer and explain its various modes of operation. 5
- (b) Explain the operation of a full wave diode bridge rectifier with diagrams. 5
10. (a) What are shift registers ? What are the different types of shift registers ? Explain any two. 5
- (b) Draw the diode ROM matrix and a basic RAM cell. 5

11. (a) Draw and explain the circuit diagram of DAC and ADC. 6
- (b) Describe and explain De Morgan's Theorems. 4
-