

**DIPLOMA – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI)**

**Term-End Examination**

**00306**

**December, 2014**

**BIELE-005 : INDUSTRIAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

---

**Note :** Attempt any **five** questions. Question no. 1 is **compulsory**. All questions carry equal marks. Missing data may be suitably assumed.

---

---

1. Attempt all objective type questions : 7×2=14

(a) In a BJT

(i)  $\beta = \alpha / (\alpha + 1)$

(ii)  $\beta = \alpha / (\alpha - 1)$

(iii)  $\alpha = \beta / (\beta - 1)$

(iv)  $\alpha = (\beta + 1) / \beta$

(b) Secondary breakdown occurs in

(i) MOSFET but not in BJT

(ii) Both MOSFET and BJT

(iii) BJT but not in MOSFET

(iv) None of these

- (c) On-state voltage drop across a thyristor used in a 250 V supply system is of the order of
- (i) 100 – 110 V
  - (ii) 240 – 250 V
  - (iii) 1 to 1.5 V
  - (iv) 0.5 to 1 V
- (d) A forward voltage can be applied to an SCR after its
- (i) anode current reduces to zero
  - (ii) gate recovery time
  - (iii) reverse recovery time
  - (iv) anode voltage reduces to zero
- (e) In a 1- $\phi$  full converter, for continuous conduction, each pair of SCRs conduct for
- (i)  $\pi - \alpha$
  - (ii)  $\pi$
  - (iii)  $\alpha$
  - (iv)  $\pi + \alpha$
- (f) In controlled rectifiers, the nature of load current is continuous or discontinuous
- (i) does not depend on type of load and firing angle delay
  - (ii) depends both on the type of load and firing angle delay
  - (iii) depends only on the type of load
  - (iv) depends only on the firing angle delay

- (g) In a 3- $\phi$  half wave rectifier, DC output voltage is 230 V. The peak inverse voltage across each diode is
- (i) 481.7 V
  - (ii) 460 V
  - (iii) 345 V
  - (iv) 230 V
2. (a) Explain the safe operation area for power transistor.
- (b) Compare MOSFET with BJT. 7+7=14
3. Write short notes on the following :  $4 \times 3 \frac{1}{2} = 14$
- (i) GTO
  - (ii) DIAC
  - (iii) IGBT
  - (iv) MOS controlled thyristors
4. (a) Explain two transistor model of SCR.
- (b) Explain resistor capacitor full wave trigger circuit for SCR. 7+7=14
5. (a) Explain resonant-pulse commutation turn-off circuit for SCR.
- (b) A resonant-pulse commutation circuit has  $C = 20 \mu\text{F}$  and  $L = 5 \mu\text{H}$ . Initial voltage across capacitor is  $V_s = 230 \text{ V}$ . For a constant load current of 300 A, calculate the
- (i) conduction time for the auxiliary thyristor.
  - (ii) voltage across the main thyristor when it gets commutated. 7+7=14

6. (a) Explain 3- $\phi$  Delta-Wye bridge rectifier.
- (b) A 1- $\phi$  mid-point SCR converter supplies constant load current of 5 A when the triggering angle is maintained at  $35^\circ$ . The input voltage to converter is 220 V at 50 Hz. The turns ratio from primary to each secondary is 0.5. Determine the load voltage and input power factor. 7+7=14
7. (a) A 1- $\phi$  semi-converter delivers power to RLE load with  $R = 5 \Omega$ ,  $L = 10 \text{ mH}$  and  $E = 80 \text{ V}$ . The AC source voltage is 230 V, 50 Hz. For a continuous conduction, find the average value of output current for a firing angle delay of  $50^\circ$ .
- (b) An RL load is fed from 1- $\phi$  supply through a thyristor. Derive an expression for load current in terms of supply voltage, frequency, R and L. Indicate time limit during which this solution is applicable. 7+7=14
-