

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

00386

December, 2014

BIELE-012 : ELECTRONIC SWITCHING CIRCUITS

Time : 3 hours

Maximum Marks : 70

***Note :** Attempt any **seven** questions. All questions carry equal marks. Missing data, if any may be suitably assumed.*

1. Give the circuit diagram of any two digital-to-analog converter circuits. Also explain the operation of any one of the above mentioned circuits. 5+5=10

2. What are the points of difference between a latch and a flip-flop ? Explain with the help of a neat diagram the operation of a D-FF and a T-FF. 3+7=10

3. Design the clocked sequential circuit whose state diagram is shown in Figure 1. 10

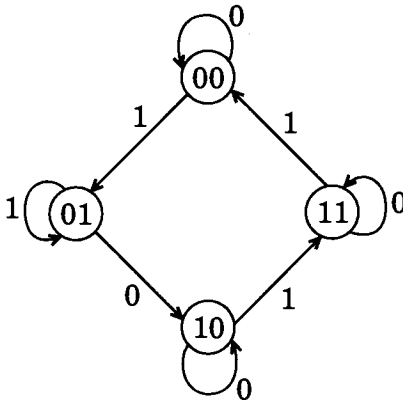


Figure 1

4. Define the term 'Definite State Model'. What are the various capabilities and limitations of finite state machines? 3+7=10
5. Design a 3-bit counter using JK flip-flops. 10
6. What are asynchronous sequential circuits? Explain the concept of timing diagram, state diagram and flow table as applicable to asynchronous sequential circuits. 3+7=10
7. Explain the steps involved in the design of hazard free combinational networks. 10
8. What are the properties of symmetric functions? Explain the process of identification and synthesis of symmetric functions. 5+5=10

9. Draw an ASM chart and state diagram for a full subtractor circuit.

10

10. Write short notes on any *two* of the following :

2×5=10

- (a) Shift Registers
- (b) Ripple Counters
- (c) Synchronous Sequential Circuits

