

**DIPLOMA IN ELECTRICAL ENGINEERING  
(DELVI) / ADVANCED LEVEL CERTIFICATE  
COURSE IN ELECTRICAL ENGINEERING  
(ACELVI)**

**00925**      **Term-End Examination**  
**December, 2014**

**BIEE-030 : INDUSTRIAL DRIVES AND  
CONTROLS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt any **five** questions. All questions carry equal marks. Question no. 1 (objective type) is **compulsory**. Draw neat and clean diagrams, if any required.*

---

1. Attempt all objective type questions. 7×2=14
- (a) A full converter feeding a DC motor
- (i) requires a FWD to conduct the motor current during the period all SCR's are OFF.
  - (ii) requires a FWD to reduce the current to be conducted by the SCR's.
  - (iii) does not require FWD as there is no period when the motor is disconnected from the supply.
  - (iv) does not require FWD as the freewheeling action is performed by SCR's themselves.

- (b) Which of the following converters can feed power in any of the four quadrants ?
- (i) Semi-converter
  - (ii) Full converter
  - (iii) Dual converter
  - (iv) Combination of semi and full converters
- (c) The advantage of the tachometer speed control method for DC motor is that, it senses
- (i) back e.m.f.
  - (ii) armature current
  - (iii) armature voltage
  - (iv) speed
- (d) For DC motors, dual converter is used to obtain
- (i) reversible speed control
  - (ii) regenerative braking
  - (iii) plugging
  - (iv) All of the above
- (e) A DC chopper circuit controls the average voltage across the DC motor by
- (i) controlling the input voltage
  - (ii) controlling the field current
  - (iii) controlling the line current
  - (iv) continuously switching ON and OFF the motor for fixed duration of  $t_{ON}$  and  $t_{OFF}$  respectively

(f) Variable voltage fixed frequency supply can be obtained from

- (i) 3-phase cyclo converter
- (ii) AC chopper
- (iii) 3-phase inverter
- (iv) None of the above

(g) In a 3-phase induction motor, the general speed control method used is the

- (i) fixed voltage fixed frequency method
- (ii) variable voltage variable frequency method
- (iii) fixed voltage variable frequency method
- (iv) None of the above

2. (a) Explain how a thyristor bridge can be used for speed control of DC shunt motor.

(b) List out the applications of phase control converters. 7+7=14

3. (a) How do you specify an SCR and what are its important ratings ?

(b) Explain the difference in operation of a semi-converter and full converter with the help of waveform analysis. 7+7=14

4. (a) How does a FWD (freewheeling diode) affect the performance of a DC motor drive? Explain.
- (b) Describe the operation of a DC chopper circuit. How is it able to regulate the DC voltage level? 7+7=14
5. (a) Explain how a DC motor speed control can be obtained using a chopper.
- (b) Draw the waveforms for full converter series motor drive. 7+7=14
6. (a) Describe the way to control the speed of an induction motor by varying the frequency. What quantity should remain relatively constant over most of the operating range?
- (b) Compare a DC motor thyristor drive with an induction motor thyristor drive. 7+7=14
7. (a) Explain the difference between a voltage-source-inverter drive and a current-source-inverter drive for an induction motor.
- (b) Explain the principle of PWM of an inverter. How does it lead to lower harmonic content of the AC voltage compared to other methods of firing the inverter circuit? 7+7=14

8. Write short notes on any **four** of the following :  $4 \times 3 \frac{1}{2} = 14$

- (a) 1-phase full wave converter feeding a separately excited DC motor
  - (b) Electric braking and heating, cooling of motors
  - (c) Stator voltage control of induction motor
  - (d) Speed-torque characteristics and expressions for DC series motor
  - (e) Differences between diode rectifier and SCR rectifier
  - (f) AC voltage controller
-