

**B.Tech. DECVI / DELVI / DCSVI / ACECVI /  
ACELVI / ACCSVI**

**Term-End Examination**

**December, 2014**

00435

**OIEE-001 : BASICS OF ELECTRICAL ENGINEERING**

*Time : 2 hours*

*Maximum Marks : 70*

---

**Note :** *There are **eight** questions. Attempt any **five** questions including question no. 1 which is **compulsory**. All questions carry equal marks. Use of scientific calculator is allowed.*

---

---

1. This part contains objective type questions. Select most appropriate option. 7×2=14

(a) kWh is the unit of

(i) Voltage


(ii) Power

(iii) Energy

(iv) None of these

(b) The current  $I_o$  of the Figure 1 is

- (i) 6 A
- (ii) - 6 A
- (iii) 34 A
- (iv) - 34 A

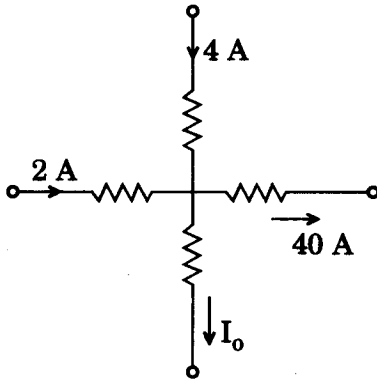

*Figure 1*

(c) The Power Factor of RC series circuit is

- (i) Leading
- (ii) Lagging
- (iii) 0
- (iv) None of these

- (d) The imaginary part of impedance is called
- (i) Resistance
  - (ii) Reactance
  - (iii) Susceptance
  - (iv) None of these
- (e) According to Fleming's left hand rule, the thumb represents the direction of
- (i) Field
  - (ii) Current
  - (iii) Force
  - (iv) Motion
- (f) Reactive Power is measured in
- (i) Watts
  - (ii) VA
  - (iii) VAR
  - (iv) None of these
- (g) In a Y – Y system a line voltage of 220 V produces a phase voltage of
- (i) 220 V
  - (ii) 127 V
  - (iii) 381 V
  - (iv) None of these

2. (a) Explain the star-delta transformation and vice-versa. 7
- (b) Find the current 'I' for the circuit shown in Figure 2 by using Superposition Theorem. 7

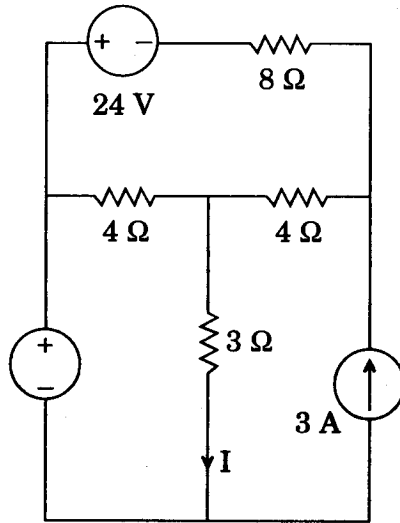


Figure 2

3. (a) State the Norton's Theorem and explain the procedure to analyze the electrical network. 7
- (b) Explain the construction, working and application of Nickel-Cadmium cell. 7
4. (a) Derive the relation for the force per unit length between two infinitely-long, parallel, straight conductors carrying current. 7

- (b) An iron ring of mean circumference equal to 80 cm is uniformly wound with 500 turns of a wire. When a current of 1 A is passed through the coil, a flux density of 1.1 T is produced in the iron. Calculate relative permeability of the iron. 7

5. (a) A conductor of 1.5 m length moves at right angles to a uniform magnetic field of flux density 1 Tesla with a velocity of 100 m/s. Calculate the e.m.f. induced in it and also find the value of induced e.m.f., when the conductor moves at an angle of  $30^\circ$  to the direction of field. 7

- (b) Determine the phasor currents  $I_1$  and  $I_2$  in the circuit of Figure 3. 7

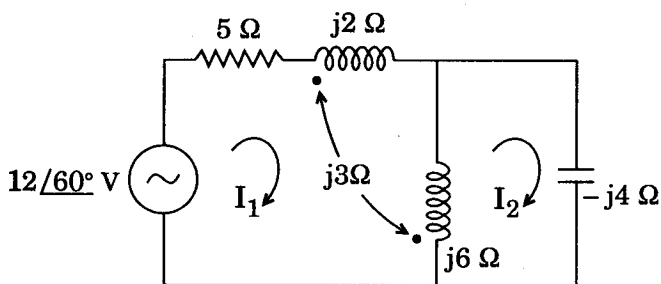


Figure 3

- 6. (a)** The two a.c. voltages are represented by  
 $v_1(t) = 30 \sin(\omega t + 45^\circ)$ ,  $v_2(t) = 60 \sin(\omega t + 60^\circ)$ .  
Calculate the resultant voltage  $v(t)$ . Also  
draw the Phasor diagram. 7
- (b)** Define the following terms : 7
- (i) Frequency
  - (ii) Amplitude
  - (iii) Time Period
  - (iv) Instantaneous Value
  - (v) Average Value
  - (vi) RMS Value
- 7. (a)** What is three-phase system ? How can we  
generate three-phase voltage ? Give its  
necessity and advantages. 7
- (b)** A balanced delta-connected load of  
impedance  $16 + j12 \Omega$  per phase is  
connected to a three-phase 400 V supply.  
Find the phase current, line current, power  
factor and total power. 7

8. Write short notes on any **four** of the following :

$$4 \times 3 \frac{1}{2} = 14$$

- (a) Ohm's Law
  - (b) Lenz's Law
  - (c) Fleming's left hand rule
  - (d) Fleming's right hand rule
  - (e) Primary cell and Secondary cell
  - (f) Superposition Theorem
-