

B.Sc. (NAUTICAL SCIENCE)**Term-End Examination****December, 2015****BNA-013 : ELECTRICITY AND ELECTRONICS***Time : 2 hours**Maximum Marks : 70*

Note : Attempt **three** questions from each section.
Question no. **1** and **5** are **compulsory**.
Non-programmable scientific calculator is allowed.

SECTION A

1. (a) With the help of a neat diagram, explain the principle, construction and working of D.C. Generator. 10
- (b) A 50 kVA, single phase transformer has 500 turns on the primary and 100 turns on the secondary. The primary is connected to 2100 V, 50 Hz supply. Calculate : 5
- (i) The secondary voltage for open circuit
- (ii) The current flowing through the two windings on full load
- (iii) The peak value of flux

2. (a) State and explain Kirchoff's laws with example. 5

(b) Using node voltage method, find the current in $3\ \Omega$ resistance for the network shown in Figure 1. 5

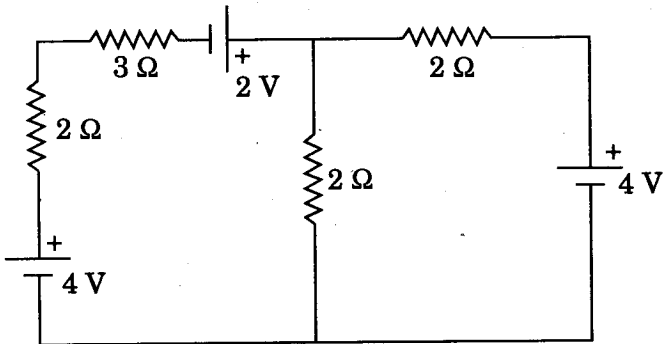


Figure 1

3. (a) What do you mean by an ideal ammeter? How do you convert a given galvanometer into an ammeter? Explain briefly. 5

(b) A moving coil meter has a resistance of $2\ \Omega$ and gives full scale deflection with $10\ \text{mA}$. Show how it can be used to measure voltage up to $250\ \text{V}$. 5

4. (a) Discuss the concept of self and mutual inductance. 5

(b) In a given $R-L$ circuit $R = 2.5\ \Omega$ and $L = 0.2\ \text{H}$. Find the current through the circuit and power factor, if an alternating voltage $v = 230 \angle 30^\circ\ \text{V}$ having frequency $50\ \text{Hz}$ is applied across the circuit. 5

SECTION B

5. (a) What is the need of modulation ? Explain the modulation index, upper and lower side band frequencies in case of amplitude modulation. 10
- (b) Explain the circuit operation of full wave bridge rectifier with proper waveshapes. 5
6. (a) What is a transistor ? Explain input and output characteristics of an NPN transistor in a common base configuration. 5
- (b) The current gain of a transistor in a common base arrangement is 0.95. Find the voltage gain and power gain, if the load resistance of the output circuit is 500 k Ω and input resistance is 100 Ω . 5
7. (a) Write a short note on electromagnetic waves. 5
- (b) The pulse repetition frequency (PRF) of a pulsed radar is 750 Hz. Find the maximum range in kilometers that the radar can detect a target. Also determine the range in miles (nmi). 5
8. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) LDR
- (b) Temperature Measurement
- (c) Transducers
-