

01161

No. of Printed Pages : 4

ET-202(B)

**B.Tech. Civil (Construction Management) /
B.Tech. Civil (Water Resources Engineering)**

Term-End Examination

December, 2015

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours


Maximum Marks : 70

Note : Answer any five questions in all.

1. (a) Explain the following terms pertaining to AC wave : 6
 - (i) Peak and Average value of sinusoidal current
 - (ii) Effective or r.m.s. value
- (b) What is superposition theorem ? Give an example using a circuit diagram. 6
- (c) Draw the block diagram of any basic feedback control system and write the transfer function for this. 2
2. (a) Explain resonance in series RLC circuit and draw the resonance curve. 6

- (b) What is KVL ? Given that $E_1 = 15 \text{ V}$, $E_2 = 10 \text{ V}$, $V_s = 20 \sin 500 t$, find the current 'i' in the following circuit :

6

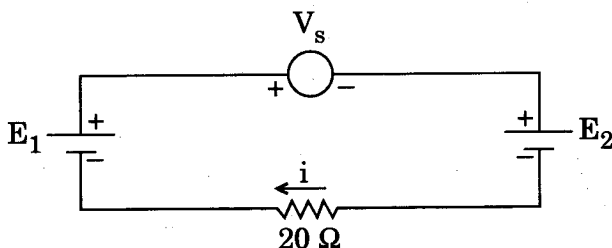

- (c) A practical voltage source can be converted into an equivalent practical current source. Draw an equivalent circuit diagram for this. 2
3. (a) Explain the necessity for power factor correction. What are the different methods for power factor correction ? 6
- (b) What are the basic components used in electrical installations ? State briefly the function of each component. 6
- (c) What is the significance of equivalent circuits ? 2
4. (a) Draw and explain the speed-torque characteristics of a d.c. series motor. 6
- (b) A d.c. machine generates an armature voltage of 220 V on no load at 1000 r.p.m., the field current being 2 A. The armature resistance is 0.5 Ω . Find its speed when it draws a current of 5 A as motor from 220 V supply. (Neglect armature reaction and brush voltage drop) 6

- (c) A Lissajous pattern obtained on a CRO screen has $f_y = 50$ Hz. Number of touching points on a horizontal tangent = 5 and the number of touching points on a vertical tangent = 3. Find f_x . 2
5. (a) Explain any four applications of op-amp with relevant circuit diagrams. 6
- (b) Discuss the different types of flip-flops used in digital circuits. 6
- (c) Draw a circuit diagram of Wien Bridge Oscillator. 2
6. (a) What are the different components of power loss in a transformer ? How is the efficiency of a transformer calculated ? 6
- (b) A 3-phase induction motor is wound for 4 poles and is supplied from 50 Hz system. Calculate : 6
- (i) Synchronous speed
- (ii) Rotor current frequency when the rotor runs at 1200 r.p.m.
- (c) Draw the $v - i$ characteristics of a reverse biased p-n junction. 2

7. (a) How can transistor (BJT) be used as amplifier and switch ? 6
- (b) What is meant by an interrupt in a microprocessor ? List all interrupts that are available in 8085 microprocessor. 6
- (c) Find the binary equivalent of the following : 2
- (i) $(79)_{10}$
- (ii) $(265)_{10}$
-