

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2015

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS
DESIGN**

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any seven questions. All questions carry
equal marks.*

1. (a) Draw and explain the equivalent circuit and ideal voltage transfer curve of an OP-AMP. 5
- (b) List the various electrical characteristics of an ideal OP-AMP. 5
2. Explain the closed loop configurations of an OP-AMP in detail with a suitable diagram. 10

3. (a) For a differentiator circuit, input is a sinusoidal voltage of peak value 5 mV and frequency 1 kHz. Determine the output voltage, if $R_F = 100 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$. 5
- (b) Explain the various effects of drift parameters. Explain in brief. 5
4. (a) What is an Instrumentation amplifier ? List the applications of this amplifier. 5
- (b) Explain the voltage to current converter with grounded load. Is there any limitation with grounded load size ? 5
5. (a) Differentiate between Clippers and Clampers using OP-AMP. Give applications of each. 5
- (b) What is the difference between slew rate and transient response ? 5
6. What is a comparator ? List the important characteristics of comparator and explain them. 10
7. Draw the schematic diagram of a saw-tooth wave generator. Also draw its input and output waveforms. 10

8. List the various modes of operation of multi-vibrator. Explain any one in detail with proper diagram and waveforms. 10
9. Define the filter order and poles. Derive the expression for transfer function of sallen key low pass filter. 10
10. Write short notes on any *two* of the following : 2×5=10
- (a) Grounding and Shielding techniques
 - (b) Sample and Hold circuit
 - (c) VCO and its applications
-