

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2015

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any *seven* questions. All questions carry equal marks. Assume any missing data suitably.

1. (a) State and prove De Morgan's Theorems. 5
(b) Differentiate between ROM, PLA and PAL. 5
2. (a) Write and explain excitation table for D flip-flop. 5
(b) Design a half adder circuit using gates. 5
3. (a) Explain the concept of PAL. 5
(b) Design and explain 4-bit comparator. 5
4. (a) Realize the following function using 8 : 1 multiplexer : 5
$$F(A, B, C, D) = \sum m (0, 1, 2, 3, 11, 12, 14, 15).$$

(b) Explain the Master-Slave JK flip-flop. 5

5. (a) What is the difference between Encoders and Decoders ? 5
- (b) What is the race-around condition in JK flip-flop ? How can it be overcome ? 5
6. (a) What is the difference between Static RAM and Dynamic RAM ? 5
- (b) Explain the working of MOSFET as switch. 5
7. (a) Simplify the logic function using Quine-McCluskey method : 5
 $f(A, B, C, D) = \pi M (2, 7, 8, 9, 10, 11, 12)$.
- (b) Design a BCD to seven segment decoder using PROM. 5
8. (a) Explain the various specifications of digital ICs. 5
- (b) Explain a ROM array and explain its working principle. 5
9. Design a 3-bit up/down counter with a control bit C. Use JK flip-flops. 10
10. Write short notes on any **two** of the following : $2 \times 5 = 10$
- (a) ASCII Code
- (b) ALU
- (c) PROM
- (d) MOS as a switch