

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2015

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any *seven* questions. All questions carry equal marks.

1. (a) Draw and explain the hybrid model of NPN BJT for each configuration. 5
- (b) A common emitter configuration has $h_{ie} = 2 \text{ k}\Omega$, $h_{fe} = 100$, $h_{re} = 10^{-5}$ and $h_{oe} = 25 \mu\text{A/V}$. If $R_S = 1 \text{ k}\Omega$ and $R_L = 1 \text{ k}\Omega$, determine the voltage gain and current gain. 5
2. Draw CE amplifier and its h-parameter equivalent circuit. Derive the expressions for input and output impedance, voltage gain and current gain. 10

3. Explain RC coupled amplifier and its frequency response with suitable diagrams. 10

4. Draw the hybrid-II model of BJT and derive expressions for the analysis of transistor using this model. 10

5. (a) Differentiate between power amplifier and voltage amplifier. 5
- (b) Explain Class A, B and AB power amplifiers. Which one has better efficiency ? 5

6. (a) Define Q-factor of tuned circuit and discuss the merits and demerits of tuned circuit. 5
- (b) Compare single tuned and double tuned amplifiers. Also discuss the frequency response of single tuned amplifier. 5

7. (a) Define the feedback concept and explain the characteristics of positive and negative feedback. 5
- (b) Draw various feedback topologies. Mention the applications of feedback. 5

8. Explain RC phase shift oscillator and derive the expression for frequency of oscillations. 10

- 9.** Draw the block diagram of IC 555 timer and explain its any one mode of operation with suitable waveforms. **10**
- 10.** Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) Cascode amplifier
 - (b) CE short circuit current gain
 - (c) Analysis and design of Class C amplifier
-