

00968

No. of Printed Pages : 3

**BIEL-011**

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**December, 2015**

**BIEL-011 : LINEAR INTEGRATED CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any seven questions. All questions carry equal marks. Missing data, if any, may be suitably assumed. Use of scientific calculator is permitted.*

---

---

1. Draw the circuit diagram of a modified BJT current source and derive an expression for its current gain and output resistance. 10
2. Give the schematic symbol of an op-amp specifying the functions of each pin. Also draw the block diagram of an op-amp and briefly describe the function of each block. 10

3. Define the terms – SVRR and CMRR. Briefly explain the procedure for determining the CMRR value of an op-amp. 5+5=10
4. Draw the high frequency equivalent circuit of an op-amp. Derive an expression for the open-loop voltage gain as a function of frequency. 4+6=10
5. Derive an expression for the output voltage of a non-inverting adder amplifier using op-amp having three inputs. Also draw its circuit diagram. 10
6. Draw the circuit diagram of a circuit voltage-to-current converter with grounded load and floating load. Also derive an expression for the output voltage of the two circuits. 5+5=10
7. Give the circuit diagram of a second-order Butterworth low-pass filter. Derive an expression for its transfer function and hence determine the value of various filter parameters. 3+7=10
8. Give the circuit diagram of a square wave generator using an op-amp. Also derive an expression for the frequency of output waveform. 4+6=10

9. Explain the operation of a sample and hold circuit with the help of a neatly labelled diagram. 10

10. Write short notes on any *two* of the following:  $2 \times 5 = 10$

(a) Voltage-Controlled Oscillation

(b) Anti-Logarithmic Amplifier

(c) Level Translator

---