

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2015

BIEL-019 : POWER ELECTRONICS

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. Draw neat waveforms and circuit diagrams. Use of scientific calculator is allowed. Missing data, if any, may be suitably assumed.*

1. Describe the working of a single-phase full converter in the inverter mode with RLE load. Illustrate your answer with waveforms for source voltage, E , load voltage and current, source current, current through and voltage across SCR. Assume continuous conduction. Also find the circuit turn-off time. Should the average output voltage be more than E during inverter operation ? Discuss.

10

2. A single phase semi-converter feeds power to RLE load. For discontinuous load current, draw the source voltage, output voltage, load current, source current and freewheeling diode current waveforms as a function of time, when the
- extinction angle $\beta > \pi$, and
 - extinction angle $\beta < \pi$ with $V_n \sin \beta < E$. 10
3. A step-down chopper, fed from 220 V d.c., is connected to RL load with $R = 10 \Omega$ and $L = 150 \text{ mH}$. Chopper frequency is 1250 Hz and duty cycle is 0.5. Calculate the
- minimum and maximum values of load current,
 - maximum value of ripple current,
 - average and rms values of load current, and
 - rms value of chopper current. 10
4. Show that the performance of a single-phase full converter with the help of typical current and voltage waveforms as effected by source inductance is given by the relation

$$\cos(\alpha + \mu) = \cos \alpha - \omega L_s I_0 / V_m$$

where the symbols have their usual meaning. 10

5. The turn-off process in a GTO can be described with its two-transistor model. Explain this in detail. 10
6. Discuss the principle of working of a three-phase bridge inverter with an appropriate circuit diagram. Draw and explain the phase and line voltage waveforms on the assumption that each thyristor conducts for 120° . 10
7. A series motor used for a rapid transit system is fed through a d.c. chopper. The series motor has total circuit resistance of 2Ω and inductance of 2 mH . What external inductance should be inserted in series with the armature circuit in order to limit the per unit ripple in armature current to 10% for a duty cycle of 0.5 ? The chopping frequency is 1 kHz. 10
8. Describe how the speed of a separately excited d.c. motor is controlled through the use of two 3-phase full converters. Discuss how two-quadrant drive can be obtained from this scheme. 10
9. Describe the stator-current control method for the speed control of a 3-phase induction motor. 10

10. Write short notes on any *two* of the following : *2×5=10*

- (a) Commutation Techniques
 - (b) Power MOSFET
 - (c) Synchronous Drives
-