

00101

No. of Printed Pages : 3

BIEE-004

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

December, 2015

BIEE-004 : ELECTRICAL MACHINES-I

Time : 3 hours

Maximum Marks : 70

*Note : Answer any **five** questions. All questions carry equal marks. Use of scientific calculator is allowed.*

1. Write short notes on any *two* of the following : $2 \times 7 = 14$
 - (a) Four-point starter
 - (b) Compound d.c. generator
 - (c) Auto-transformer

2. Discuss the cross-magnetising and demagnetising effects of armature reaction in d.c. machine. Also, explain the methods of decreasing the effects of armature reaction in detail. 14

3. (a) Why is d.c. series motor not started at no load ? Justify your answer with suitable characteristic. 7

- (b) A 250 V compound generator has armature, series-field and shunt-field resistances 0.4Ω , 0.2Ω and 125Ω , respectively. If this generator supplies 10 kW at rated voltage, determine the emf generated in the armature when the machine is connected as long shunt. 7
4. (a) Discuss the speed control of d.c. motor using Ward-Leonard method. 7
- (b) Explain the significance of back emf in a d.c. motor. 7
5. (a) Explain the open circuit test of a single-phase transformer with the help of a connection diagram. 7
- (b) A 200 kVA 11000/400 V, Δ -Y transformer, gave the following no-load test :
- Test Voltage = 400 V
- Test Current = 9 A
- Power Consumed = 1.5 kW.
- Determine the equivalent circuit parameter referred to high voltage side. 7
6. (a) Establish the condition for determining maximum efficiency of a transformer. 7
- (b) A 10 kVA, 2500/250 V, 1- ϕ transformer gave the following test results :
- Open-circuit test : 250 V, 0.8 A, 50 W
- Short-circuit test : 60 V, 3 A, 45 W.
- Calculate the efficiency at half full load at 0.8 p.f. 7

7. (a) Explain the working of a tap changer transformer using schematic diagram. 7
- (b) Explain power and distribution transformers in detail. 7
-