

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

Term-End Examination

December, 2015

**BIEE-008 : ELECTRO-MECHANICAL ENERGY
CONVERSION - I**

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **five** questions. All questions carry equal marks. Use of scientific calculator is allowed.*

1. (a) Explain Electro-mechanical Energy Conversion system with the help of a block diagram. 7
- (b) Discuss briefly about torque production in rotating machine. Also, give examples of singly excited and doubly excited magnetic field system. 7

2. (a) Describe the working of a three-point starter for d.c. shunt motor, with the help of a neat diagram. 7
- (b) Compare and distinguish a three-point starter with a four-point starter. 7
3. (a) A 500 V series motor takes current of 180 A to develop 80 kW. The armature and series field resistances are 0.1 ohm and 0.04 ohm respectively. If the output is reduced to 40 kW, find the input current and efficiency. 7
- (b) Describe the Ward Leonard method of speed control of d.c. motor. 7
4. (a) Draw and explain the phasor diagram of a single phase transformer on inductive load. 7
- (b) A 10 kVA, 400/200 V single-phase 50 Hz transformer has a maximum efficiency of 92% at 80% of full load at unity p.f. Determine the efficiency at full load at 0.8 p.f. lagging. 7
5. (a) What is Sumpner's test ? Draw a circuit diagram to conduct this test and explain its operation. 7
- (b) What is an auto-transformer ? Derive an expression for saving of copper, when an auto-transformer is used. 7

6. (a) Draw and explain Scott connection of a transformer. 7
- (b) List the advantages and disadvantages of 3-phase transformer. 7
7. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Voltage Regulation of Transformer
- (b) Swinburne's Test
- (c) Armature Reaction in DC Machine
-