

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

**December, 2015**

**BIEE-014 : NETWORK THEORY**


*Time : 3 hours*

*Maximum Marks : 70*

**Note :**

- (i) *Attempt any five questions.*
- (ii) *Use of scientific calculator is allowed.*
- (iii) *Missing data, if any, may be suitably used.*

1. (a) Explain the following terms with their main difference : 6
- (i) Mesh and Loop
  - (ii) Cell and Battery
  - (iii) Tree and Co-tree
- (b) Draw the graph of the network shown in Figure 1. Select a suitable tree to write tie-set schedule. Hence find the three loop currents. 8

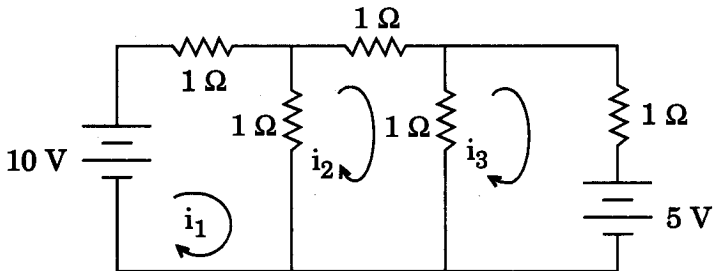

*Figure 1*

2. (a) Derive an expression for maximum power transfer theorem for an a.c. circuit. 10
- (b) In the network shown in Figure 2, two voltage sources act on the load  $Z_L$ . If the load is variable, for what value will the load  $Z_L$  receive maximum power? 4

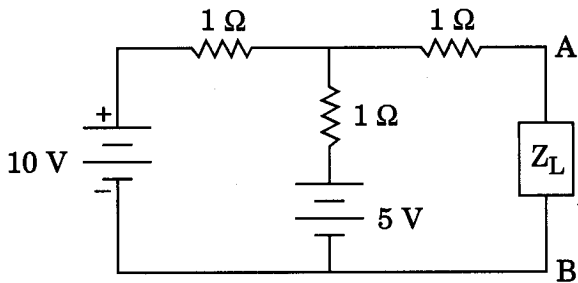


Figure 2

3. (a) State and prove Millman's Theorem. Write about its application in electrical engineering. 7
- (b) Using source conversion, find the equivalent voltage across the load terminals in the network shown below in Figure 3. 7


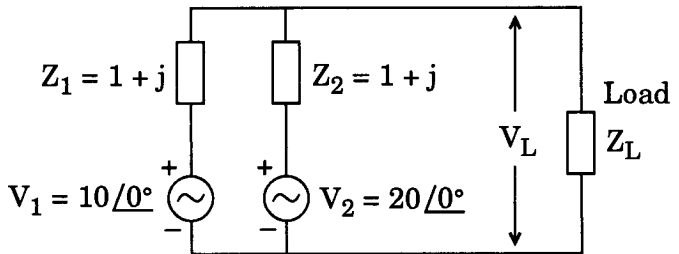



Figure 3

4. (a) What is driving point admittance ? Determine the driving point admittance  $Y_{11}(s)$  of the network shown in Figure 4. 7

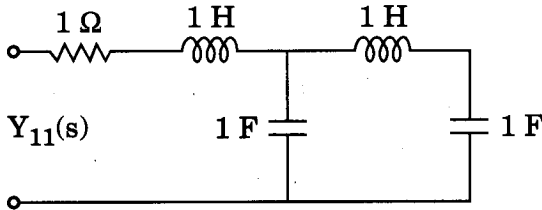

*Figure 4*

- (b) What are poles and zeros ? Give the restrictions on pole and zero location in transfer functions. 7
5. (a) Derive the condition of reciprocity for ABCD parameters. 7
- (b) Derive the condition for symmetrical network for Y parameter. 7
6. (a) Check whether the network shown in Figure 5 is reciprocal or not. 7

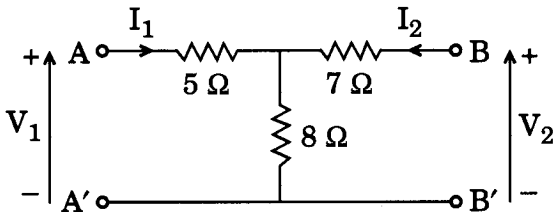

*Figure 5*

- (b) Realise the following RC driving point impedance function in Foster-II form : 7

$$z(s) = \frac{(s^2 + 4s + 3)}{(s^2 + 2s)}$$

7. Write short notes on any **two** of the following : 2×7=14

- (a) High Pass Filter
  - (b) Positive Real Function
  - (c) Active and Passive Filters
-