

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

**December, 2015**

**BIEE-017 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any **seven** questions. Assume missing data, if any.*

---

---

1. Draw a circuit that uses only one AND gate and one OR gate to realize each of the following functions : 10
  - (a)  $ABCF + ACEF + ACDF$
  - (b)  $(V + W + Y + Z)(U + W + Y + Z)$   
 $(W + X + Y + Z)$
  
2. Show how a full-adder can be converted to a full-subtractor with the addition of one inverter circuit. 10

3. Implement the following expression using a multiplexer : 10

$$F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$$

4. Implement the following functions using 3 : 8 decoder : 10

(a)  $F_1(a, b, c) = \sum m(0, 1, 3, 5, 6)$

(b)  $F_2(a, b, c) = \sum m(0, 2, 4, 7)$

5. Describe the operation of an SR flip-flop. 10

6. Discuss the working of serial in parallel out shift register with logic diagram and waveforms. 10

7. Design a sequential circuit with JK flip-flops to satisfy the following state equations : 10

$$A(t + 1) = A'B'CD + A'B'C + ACD + AC'D'$$

$$B(t + 1) = A'C + CD' + A'BC'$$

$$C(t + 1) = B$$

$$D(t + 1) = D'$$

8. Explain the instruction set of Intel 8085 microprocessor. 10

**9.** Explain the following assembler directives : *10*

(a) ASSUME

(b) DW

(c) DD

(d) DB

(e) EQU

**10.** Write a program to find out whether a given byte is in the string or not. If it is in the string, find out the relative address of the byte from the starting location of the string. *10*

---