

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination  
December, 2015**

**BIEE-018 : HIGH VOLTAGE ENGINEERING**

*Time : 3 hours*

*Maximum Marks : 70*

*Note : Attempt any seven questions. All questions carry equal marks.*

1. (a) With the help of a suitable diagram, explain the working of a cascaded voltage multiplier circuit for high voltage generation. 7
- (b) Derive an expression for ripple in a cascaded voltage multiplier circuit. 3
2. A Rogowski coil is to be designed to measure the impulse current 10 kA having a rate of change of current of 10 A/sec. The current is read by a VTVM as a potential drop across the integrating circuit connected to the secondary. Estimate the value of mutual inductance and capacitance to be connected, if the meter reading is to be 10 V for full scale deflection. Resistance has to be selected as  $2 \times 10^3$  ohms. 10

3. (a) Explain a typical series resonance circuit for the production of high voltage. 5
- (b) Explain a typical wave shaping circuit with the help of a simple diagram. 5
4. Explain the principle and working of hall generator used for the measurement of high direct current with the help of a neat sketch. 10
5. With the help of a neat labelled diagram, explain the construction and working of an electrostatic voltmeter. 5+5
6. What is dielectric loss ? Explain in detail a method for measuring the dielectric loss of a solid dielectric. 2+8
7. Explain Townsend's theory of discharge in a gaseous dielectric. Define Townsend's first and second ionization constant. 6+2+2
8. (a) How does Streamer theory remove the limitations and drawbacks of Townsend's theory ? 5
- (b) Define Paschen's law. Give the mathematical expression of Paschen's law. Where is this law used ? 2+2+1

9. (a) Explain how the radio interference can be measured with the help of a simple circuit diagram. 5
- (b) How are high voltage measurements done on circuit breakers and surge diverters? 5
10. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Thermal Breakdown
- (b) Schering Bridge
- (c) Voltage Doubler
- (d) Van de Graaff Generator
-