

**B.Tech. MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING) /
B.Tech. (AEROSPACE ENGINEERING) (BTAE)**

Term-End Examination

December, 2015

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCE**

Time : 3 hours

Maximum Marks : 70

Note : Answer five questions in all. Question no. 1 is compulsory. Answer any two questions from Section A and any two from Section B. Symbols and abbreviations have their usual meaning. Use of scientific calculator is allowed.

1. State whether the following statements are *True* or *False* : $7 \times 2 = 14$

- (a) The specific resistance depends upon the area of cross-section of the conductor only.
- (b) The unit of magnetic field (B) is Wb/m^2 .

- (c) Norton's theorem is not applicable to a.c. circuits.
- (d) The phase angle between voltage and current is 90° in case of purely resistive circuit.
- (e) BJT can be used as switch.
- (f) According to De Morgan's first theorem
- $$\overline{A + B} = \bar{A} \cdot \bar{B}.$$
- (g) The maximum data rates for RS-232 is 19.2 k baud or bits per second.

SECTION A

Attempt any two questions from this section.

2. (a) Explain the factors affecting the resistivity of conductors. What are the limitations of Ohm's law? 7
- (b) A coil with 250 turns carries a current of 2 A, and produces a flux a of 0.3 mWb. When this current is reduced to zero in 2 milliseconds, the voltage induced in a nearby coil is 60 volts. Calculate (i) self-inductance of each coil, and (ii) mutual inductance between the coils. Assume coefficient of coupling = 0.7. 7
3. (a) State the Thevenin's theorem with the help of a suitable example. 7
- (b) Explain the principle of operation of a transformer and draw the equivalent circuit of a transformer referred to the secondary side. 7

4. (a) Explain the principle of operation of a three-phase induction motor. Also, derive the relation between rotor frequency and stator frequency. 7
- (b) Find the (i) frequency of resonance, (ii) current and power factor at resonance, and (iii) Q-factor at resonance, for the circuit shown in Figure 1. 7

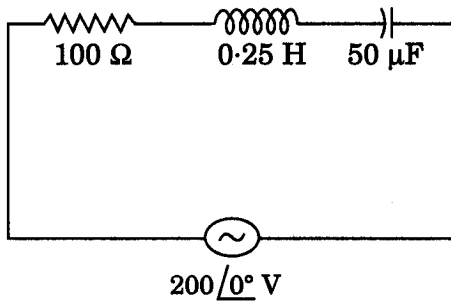


Figure 1

SECTION B

Attempt any two questions from this section.

5. (a) Explain the I – V characteristics of Zener diode and explain its working as a voltage regulator. 7
- (b) What is the full form of MODEM ? What are the basic functions of MODEM ? 7
6. (a) Draw the circuit diagram of an NPN junction transistor CE configuration and describe the static input and output characteristics. 7
- (b) Convert the following decimal numbers into binary : 7
- (i) 35
- (ii) 127
7. (a) Draw the block diagram of a computer and explain each block. 7
- (b) Write short notes on the following : 7
- (i) TRIAC
- (ii) IGBT
-