

00768

No. of Printed Pages : 5

BIEL-027

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI**

Term-End Examination

December, 2015

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Answer *five* questions in all. All questions carry equal marks. Question number 1 is **compulsory**.

1. (a) Negative feedback is used in
 - (i) Amplifiers
 - (ii) Oscillators
 - (iii) None of these
 - (iv) Both (i) and (ii)
- (b) p-n junction diode is an active device.
(True/False)
- (c) Crossover distortion is removed by
 - (i) Class A amplifier
 - (ii) Class B push-pull amplifier
 - (iii) Class AB push-pull amplifier
 - (iv) Class C amplifier

- (d) FET is a current controlled device.
(True/False)
- (e) For sustained oscillations, AB must be
- (i) Less than one
 - (ii) Greater than one
 - (iii) Equal to one
 - (iv) Greater than or equal to one
- (f) The output waveform of Schmitt trigger is
- (i) Sinusoidal
 - (ii) Triangular
 - (iii) Square
 - (iv) None of these
- (g) Which amplifier is used in Miller bootstrap time base generator ?
- (i) Common emitter
 - (ii) Emitter follower
 - (iii) Common base
 - (iv) None of these
- 7×2=14

2. (a) Explain the operation of Class AB Push-Pull amplifier with the help of a neat diagram.
- (b) Explain the operation of P-channel Enhancement Type MOSFET with the help of a suitable diagram. Also draw its drain characteristics. Explain the threshold voltage. 2×7=14
3. (a) Discuss the advantages of negative feedback in detail.
- (b) Write down the Barkhausen criterion for sustained oscillations. In a phase shift oscillator, $R_1 = R_2 = R_3 = 800 \text{ k}\Omega$ and $C_1 = C_2 = C_3 = 100 \text{ pF}$. Determine the frequency of oscillations. 2×7=14
4. (a) Find out the V_o for the following RC circuit, if step i/p is applied. Also draw the o/p waveform. (Figure 1)

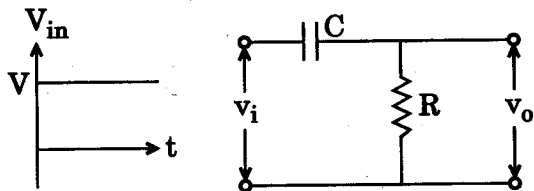


Figure 1

- (b) Determine the output waveform of the network shown in Figure 2 and calculate the PIV of each diode. $2 \times 7 = 14$

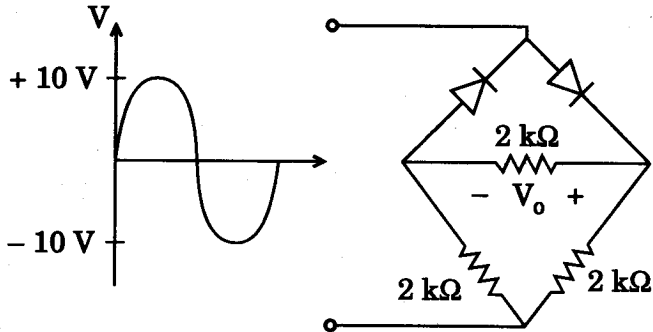


Figure 2

5. (a) Explain the operation of n-p-n transistor as a switch with the help of a suitable diagram.
- (b) Explain the operation of a Bistable Multivibrator with the help of a neat diagram. Write down its applications. $2 \times 7 = 14$
6. (a) Explain the operation of an exponential base generator with the help of a suitable diagram.
- (b) Explain the operation of a suitable time base generator which is used in CRO. $2 \times 7 = 14$

7. (a) What is the fundamental difference between Audio amplifier and Tuned amplifier ? Also explain the operation of Class A transformer coupled resistive load amplifier.
- (b) Explain the operation of a Wien Bridge oscillator with the help of a neat diagram.

$2 \times 7 = 14$

8. Write short notes on any *four* of the following :

$4 \times 3 \frac{1}{2} = 14$

- (a) Tuned Amplifier
 - (b) Power Amplifier
 - (c) JFET
 - (d) LC Oscillator
 - (e) Schmitt Trigger
 - (f) Negative Resistance Generator
 - (g) Trouble-shooting of Multivibrator
-