

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

December, 2015

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : Attempt five questions in all. Question no. 1 is compulsory.

1. Choose the correct alternative.

(a) The Laplace transform of $u(t)$ is 2

(i) $\frac{1}{s^2}$

(ii) $\frac{1}{s}$

(iii) $\frac{2}{s^3}$

(iv) 1

(b) Three inductances of 4 H each are connected in series. The equivalent inductance is 2

(i) 11 H

(ii) 64 H

(iii) 12 H

(iv) 10 H

(c) If a circuit element has the capability of enhancing the energy level of a signal passing through it, it is called a/an _____. 2

(i) passive element

(ii) active element

(iii) Both active and passive

(iv) Either passive or active

(d) The frequency that separates the pass band and the attenuation band is known as _____ frequency. 2

(e) Q-factor of a series resonating circuit is 2

(i) $Q = \frac{1}{\omega_0 RC}$

(ii) $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

(iii) Both (i) and (ii)

(iv) None of the above

(f) ABCD parameters are also known as _____ parameters. 2

(g) The current in any inductor is given by 2

(i) $L \int v(t) dt$

(ii) $\frac{1}{L} \int v(t) dt$

(iii) $L \frac{d}{dt} [v(t)]$

(iv) $L^2 \int v(t) dt$

2. (a) Calculate the power loss across the 10 Ω resistor using Thevenin's theorem for the circuit shown in Figure 1. 7

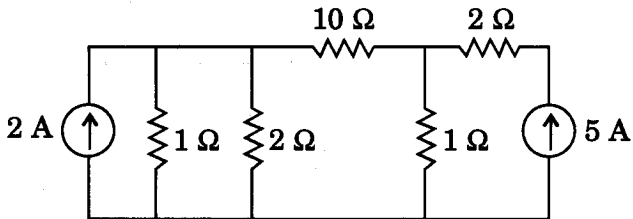


Figure 1

- (b) Find V by superposition theorem in Figure 2. 7

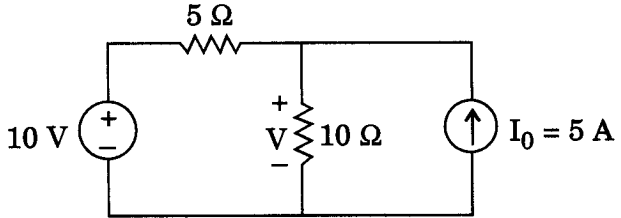


Figure 2

3. (a) A series LCR circuit has inductance of 10 mH and resistance of $2\ \Omega$. What is the value of capacitance that will produce resonance at 15.9 kHz? 6
- (b) Define figure of merit, current bandwidth, impedance and selectivity in series resonance. 8
4. (a) In a series RC circuit, the resistance is of $2\ \Omega$ while the capacitor is of $1/4\ \text{f}$. Find the transfer function of the voltage and the drop across the capacitor assuming the supply voltage to be $V_0(t) = tu(t)$. 8
- (b) Find $i(t)$ in Figure 3. Assume zero initial response. 6

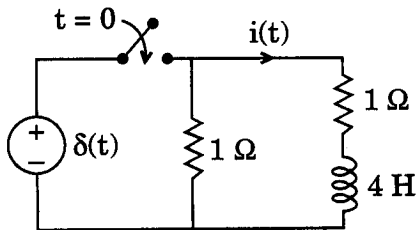


Figure 3

5. (a) Design a constant k high pass filter having $f_c = 4$ kHz and design impedance, $R_0 = 600 \Omega$ (π section). 7
- (b) Design a constant k low pass filter having $f_c = 2$ kHz and design impedance $R_0 = 600 \Omega$. Obtain the value of attenuation at 4 kHz. 7
6. (a) Obtain the transfer function $V_2(s)/V_1(s)$ in Figure 4. 7

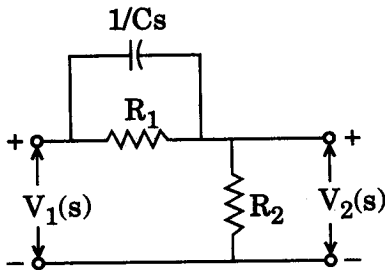


Figure 4

- (b) In the network of Figure 5, find the pole-zero plot. 7

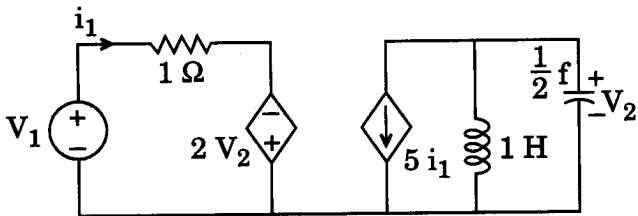


Figure 5

7. (a) Derive the Reciprocity condition of Y parameter. 7
- (b) Find the Z-parameters for the network shown in Figure 6. 7

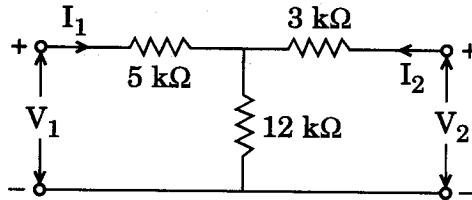


Figure 6

8. Write short notes on any **four** of the following : $4 \times 3 \frac{1}{2} = 14$
- (a) Applications of Resonance Circuits
 - (b) Norton's Theorem
 - (c) Hybrid Parameters
 - (d) Attenuators
 - (e) Parallel Resonance