

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

Term-End Examination

December, 2015

BIEL-038 : LINEAR INTEGRATED CIRCUITS

Time : 2 hours

Maximum Marks : 70

*Note : First question is **compulsory** and attempt any **four** from the rest. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, should be assumed.*

1. Choose the correct alternative. 7×2=14
- (a) The ratio of change in input offset voltage when variation in supply voltage is made is called
- (i) PSRR
 - (ii) CMRR
 - (iii) Transient response
 - (iv) Input offset voltage stability

- (b) The order of input resistance of IC-741C OP-AMP is
- (i) $10^4 \Omega$
 - (ii) $10^3 \Omega$
 - (iii) $10^5 \Omega$
 - (iv) $10^6 \Omega$
- (c) A triangle-wave oscillator consists of an OP-AMP comparator followed by a/an
- (i) Differentiator
 - (ii) Amplifier
 - (iii) Integrator
 - (iv) Multivibrator
- (d) Slew rate of an ideal OP-AMP is
- (i) 1
 - (ii) 0
 - (iii) ∞ (infinity)
 - (iv) None of these
- (e) IC-555 can be used as a/an
- (i) Differentiator
 - (ii) Integrator
 - (iii) Ramp-generator
 - (iv) Multivibrator

- (f) A notch filter is a
- (i) Wide BPF
 - (ii) Narrow BPF
 - (iii) Wide band reject filter
 - (iv) Narrow band reject filter
- (g) The output of an OP-AMP integrator is

(i) $-R_f C_1 \frac{dV_i}{dt}$

(ii) $R_1 C_F \int V_i(t) dt$

(iii) $\frac{1}{R_1 C_F} \int V_i(t) dt$

(iv) $\frac{R_1}{C_F} \int V_i(t) dt$

2. (a) Draw and explain the schematic block diagram of an OP-AMP. 7

(b) What is a practical OP-AMP ? Draw its equivalent circuit diagram. Why is R_E replaced by a constant current bias circuit in a differential OP-AMP ? 7

3. (a) What is the difference between open-loop gain and closed-loop gain of an OP-AMP ? Draw an OP-AMP circuit whose output is $V_1 + V_2 - V_3 + V_4$ and explain its operation. 7
- (b) Draw and explain the operation of a practical integrator with necessary waveforms and derivation. 7
4. (a) For the non-inverting amplifier of the given figure 1, $R_1 = 1\text{ k}\Omega$ and $R_f = 10\text{ k}\Omega$. Calculate the close-loop voltage gain of the amplifier and the feedback factor β . 7

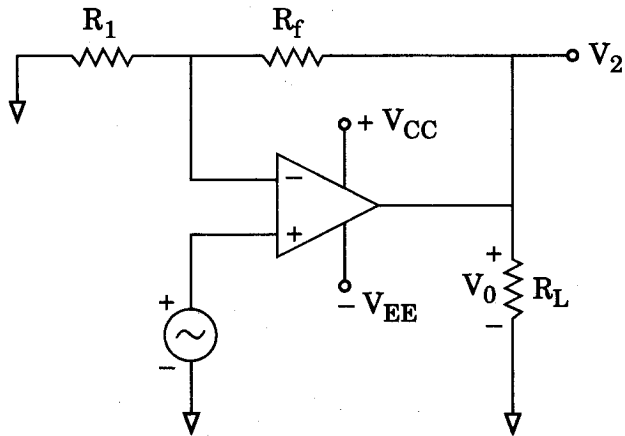


Figure 1

- (b) Draw the circuit of a voltage-to-current converter if the load is (i) Floating, and (ii) Grounded. 7

5. (a) Explain how a sawtooth waveform is generated by using a sinusoidal waveform in the OP-AMP circuitry with necessary diagrams and waveforms. 7
- (b) How can Q-factor of an active filter be improved? Draw and explain the transfer characteristics of an all pass filter. 7
6. (a) Draw and explain the operation of a second order Butterworth low pass active filter. 7
- (b) In an astable multivibrator, $R_A = 6.8 \text{ k}\Omega$, $R_B = 3.3 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$. Calculate (i) t_{HIGH} , (ii) t_{LOW} , (iii) Free running frequency, and (iv) Duty cycle. 7

7. (a) The differential input OP-AMP shown in figure 2 consists of a base amplifier of infinite gain. Show that

$$V_{\text{out}} = \frac{R_2}{R_1} (V_2 - V_1).$$

7

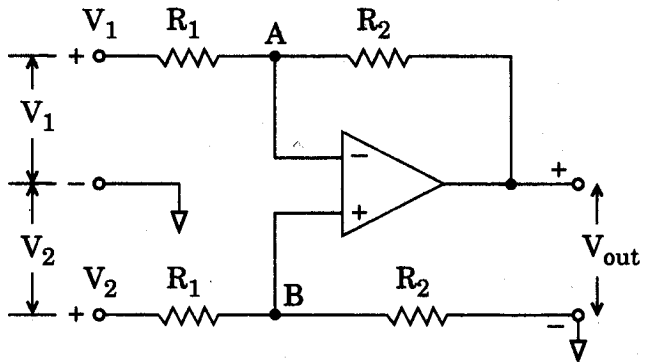


Figure 2

- (b) Write down the various applications of IC-565 (PLL). Explain any one of these. 7
8. Explain any *two* of the following : 2×7=14
- (a) Bistable Multivibrator
 - (b) Timer IC-555
 - (c) Sample and Hold Circuit