

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING (BTECVI)**

**Term-End Examination**

**December, 2015**

**BIELE-004 : RF CIRCUITS**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** *Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed.*

---

---

1. (a) Draw the equivalent circuits of transmission lines.  
(b) Derive the input impedance equation of a transmission line of length ' $l$ '.  $2 \times 5 = 10$
2. (a) Derive an expression for the 'Noise Figure' of cascaded networks.  
(b) Explain the characteristics of passive IC components at RF frequencies.  $2 \times 5 = 10$
3. Show that the ideal Class A amplifier has an efficiency of 50% and the ideal Class B amplifier has an efficiency of  $\pi/4$  or 78.5%.  $10$

4. (a) The parameters of a transmission line are  $R = 2 \Omega/\text{m}$ ,  $G = 0.5 \text{ ms/m}$ ,  $L = 8 \text{ nH/m}$  and  $C = 0.23 \text{ pf/m}$ . If the signal frequency is 1 GHz, calculate its characteristic impedance ( $Z_0$ ) and the propagation constant ( $\gamma$ ). 6
- (b) A signal propagating through a  $50 \Omega$  distortionless transmission line attenuates at a rate of 0.01 dB per metre. If this line has a capacitance of 100 PF per metre, find (i) R, (ii) L, (iii) G, and (iv)  $v_p$ . 4
5. (a) Derive the expression for a two-port network to be unconditionally stable.
- (b) Explain two-port stability criterion.  $2 \times 5 = 10$
6. (a) Explain different types of RF power amplifiers. Briefly explain each with its application point of view.
- (b) Explain the linearity consideration of RF power amplifiers.  $2 \times 5 = 10$
7. (a) What is noise ? Describe the noise models for active and passive components.
- (b) Explain the operation of diode-ring mixers.  $2 \times 5 = 10$
8. (a) Explain the basic building blocks design of a Low noise amplifier. Write the LNA topologies.
- (b) What is the difference between neutralization and unilateralization of high frequency amplifier design ?  $2 \times 5 = 10$

9. (a) Discuss about multiplier-based mixers and subsampling mixers.
- (b) Explain the operation principle of an RF oscillator by drawing its suitable diagram.
- (c) What is negative resistance oscillator ?  
Explain its principle.  $4+4+2=10$
10. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Synthesizer
- (b) Shunt-Series Amplifier
- (c) S-parameters
-