

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(DECVI)**

**Term-End Examination
December, 2015**

BIELE-006 : ELECTRONIC PRODUCT DESIGN

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions. Question no. 1 is **compulsory**. Each question carries equal marks. Use of scientific calculator is permitted.

1. Choose the correct answer : 7×2=14

(a) The device that is typically used as a stable reference voltage in a linear voltage regulator is

- (i) SCR
- (ii) Junction diode
- (iii) Varactor diode
- (iv) Zener diode

(b) The information in ROM is stored

- (i) By the user using electrical signal
- (ii) By the manufacturer during fabrication of the device
- (iii) By the user using ultraviolet light
- (iv) By the user once and only once

- (c) The dynamic regulation of a power supply is improved by increasing the value of
- (i) the choke
 - (ii) the input capacitor
 - (iii) the output capacitor
 - (iv) the bleeder resistor
- (d) The device which changes from parallel data to serial is
- (i) Counter
 - (ii) Multiplexer
 - (iii) De-multiplexer
 - (iv) Flip-flop
- (e) The number of control lines for 32 to 1 multiplexer is
- (i) 4
 - (ii) 5
 - (iii) 16
 - (iv) 6
- (f) A decoder is a
- (i) Sequential device
 - (ii) Combinational device
 - (iii) ALU
 - (iv) All of the above
- (g) The process of entering data into a ROM is called
- (i) Burning
 - (ii) Programming
 - (iii) Writing
 - (iv) Charging

2. What is the function of a voltage regulator ? Draw and explain the block diagram of regulated DC power supply. 14
3. (a) What do you mean by overcurrent ? How is overcurrent protection provided in the regulated power supply ? 7
- (b) Differentiate between Moore and Mealy machines with necessary block diagrams. 7
4. (a) Realize the following Boolean function $F(A, B, C) = \Sigma(0, 1, 3, 5, 7)$ using : 7
- (i) 8 : 1 MUX
- (ii) 4 : 1 MUX
- (b) Design Binary to Gray code converter using ROM. 7
5. (a) Design a second order unity gain high pass filter with f_0 of 7.2 kHz and Q of 0.5. 7
- (b) Explain various realization techniques of KRC filters. 7
6. (a) On what factors does the damping coefficient of a filter depend ? Explain why cascading of filters is done for higher order filter design. 7
- (b) Draw and explain the output interfacing of a DAC with PWM for analogue output using microcontroller. 7

7. (a) Write down the applications of microcontroller based data acquisition systems. 7
- (b) What are the criteria to select suitable Analog-to-Digital Converter for a microcontroller ? 7
8. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Thermal considerations
- (b) FSM-sequence generator
- (c) Frequency response simulation using software like P-SPICE etc.
-