

**B.Tech. – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**December, 2015**

**BIELE-011 : DIGITAL SYSTEM DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

---

**Note :** Attempt any **seven** questions. All questions carry equal marks.

---

1. Implement the truth table of a binary full subtractor using 4 : 1 MUX. Is MUX a programmable device? Justify your answer. 10
2. Design a 3-bit binary Up-Down counter using J-K flip-flop. Explain its operation. 10
3. What are the various controller design principles? Discuss their time and frequency considerations. 10
4. Design an asynchronous machine which changes its state in the sequence  $2 \rightarrow 4 \rightarrow 7 \rightarrow 9 \rightarrow 13 \rightarrow 15$  and repeats, when input  $X = 1$ . 10
5. How can a ROM be used for implementing the truth table of BCD to EX-3 code converter? 10

6. Write down the truth table and VHDL code for a 3-bit up/down counter. Also draw the circuit and output waveforms. 10
7. What is micro-programmed control unit ? Explain the working of a programmable controller with a block diagram. 10
8. (a) Draw a block diagram for PLA control logic and explain its working.
- (b) What is the role of ROM and PROM in micro-program control logic ? 5+5
9. Discuss an example of the use of multiplexer in system controller. Draw the block diagram. 10
10. Discuss the design of asynchronous machine. What are cycle and races in asynchronous circuits ? How can they be avoided ? 10
-