

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)**

Term-End Examination

December, 2015

BIEE-033 : ELECTRICAL CIRCUIT THEORY

Time : 2 hours


Maximum Marks : 70

Note : Attempt any **five** questions. Question no. 1 is **compulsory**. All questions carry equal marks. Use of scientific calculator is allowed. Assume missing data, if any.

1. Select the correct alternative. $7 \times 2 = 14$
- (a) Kirchhoff's law is applicable to
- (i) AC circuits only
 - (ii) DC circuits only
 - (iii) AC as well as DC circuits
 - (iv) Passive networks only
- (b) Power factor of pure inductor is
- (i) unity
 - (ii) zero
 - (iii) infinite
 - (iv) 0.707 lagging


- (c) A close path made by several branches of the network is known as
- (i) circuit
 - (ii) branch
 - (iii) junction
 - (iv) loop
- (d) Power factor of a series resonating circuit is
- (i) unity
 - (ii) zero
 - (iii) 0.707 lagging
 - (iv) 0.707 leading
- (e) As per maximum power transfer theorem, the internal resistance of a circuit should be equal to _____ for maximum power transfer to load.
- (i) cell resistance
 - (ii) load resistance
 - (iii) load inductance
 - (iv) load capacitance
- (f) In a circuit, the current is $10/\underline{-30^\circ}$ amp. Nature of the current is
- (i) leading
 - (ii) lagging
 - (iii) in phase with voltage
 - (iv) All of the above
- (g) Resistance of a 100 watt 200 volt lamp is
- (i) 100 Ω
 - (ii) 200 Ω
 - (iii) 400 Ω
 - (iv) 1600 Ω

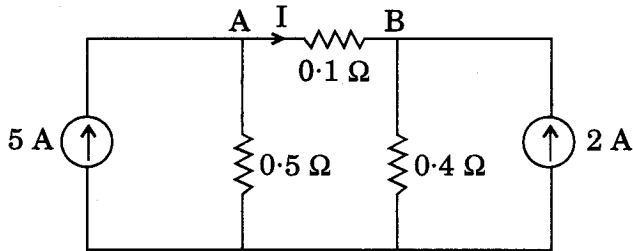2. (a) State and explain Kirchoff's voltage law with the help of an example. 7
- (b) Find out the current (I) through the 0.1Ω resistor, using Thevenin's theorem. 7



3. (a) State and explain nodal analysis with the help of a suitable example. 7
- (b) State, prove and explain maximum power transfer theorem. 7
4. (a) State the condition of series resonance. Also define and derive the Quality factor of a series resonant circuit. 2+5
- (b) A coil of resistance 100Ω and inductance 100 mH is connected in series with a 100 pF capacitor. The circuit is connected to a 10 volt variable frequency source. Calculate (i) the resonant frequency, (ii) the current at resonance, and (iii) Q-factor of the circuit. 7

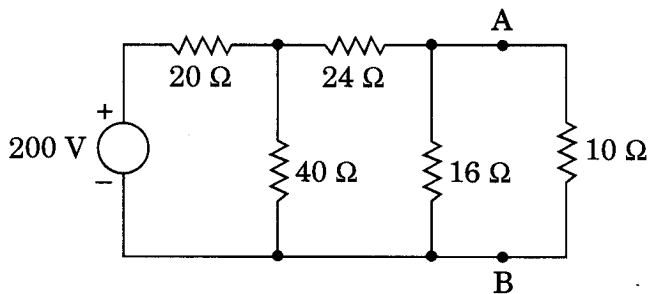5. (a) Explain power triangle and impedance triangle. Also give the formula and units of real, imaginary and apparent power in case of an a.c. circuit. 2+2+3
- (b) A resistance of $20\ \Omega$ is in series with an inductance of 0.1 henry with the terminal voltage of 230 volt 50 Hz. Find the value of current. Also calculate the phase angle between voltage and current. 7
6. (a) State and explain Superposition theorem with the help of suitable diagrams. 7
- (b) Using Norton's theorem, determine the current in the $10\ \Omega$ resistor of the given network. 7



7. Write short notes on any **two** of the following : $2 \times 7 = 14$
- (a) Delta Star Transformation
- (b) Nodal Analysis
- (c) Parallel Resonance
- (d) Duality and Dual Networks