

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)****Term-End Examination****December, 2015****BIEEE-008 : FLEXIBLE AC TRANSMISSION SYSTEM***Time : 3 hours**Maximum Marks : 70*

Note : Attempt five questions in all. All questions carry equal marks.

1. (a) What do you understand by FACTS devices ? Mention their objectives in power system advancement. 7
- (b) Discuss in detail the loadability characteristics of overhead lines. 7
2. (a) Compare the 'SVC' and 'STATCOM'. 7
- (b) Give the principle and working of a 'TSC' shunt compensator with a suitable diagram. 7
3. (a) Explain 'TCR' compensator and its working. 7
- (b) With relevant derivations and diagrams, show that the line length affects the voltage and reactive power of uncompensated line under loading condition. 7

4. (a) Discuss all functional capabilities of 'UPFC' with suitable diagrams. 7
- (b) Explain the construction and working of a Static Series Synchronous Compensator (SSSC). 7
5. (a) Explain Thyristor Controlled Braking Resistor (TCBR) in terms of equal area criterion for transient stability. 7
- (b) Explain the importance of Interline Power Flow Controller (IPFC) in power systems. 7
6. (a) Draw the basic thyristor voltage regulator configuration for continuous control of output voltage. 7
- (b) Write various difficulties associated with the reactive power flow on lines. 7
7. Write short notes on any *two* of the following : 2×7=14
- (a) Thyristor Controlled Voltage Regulator
- (b) Battery Energy Storage Systems
- (c) Thyristor Controlled Current Limiter
-