

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)****Term-End Examination****December, 2015****BIEEE-016 : INDUSTRIAL DRIVES***Time : 3 hours**Maximum Marks : 70*

---

**Note :** (i) *Attempt any seven questions.*(ii) *All questions carry equal marks.*(iii) *Missing data, if any, may be suitably assumed.*(iv) *Use of scientific calculator is permitted.*

---

---

1. What is electric drive system ? Draw its block diagram and explain its working. 10
2. (a) What are the advantages of a.c. drives over d.c. drives ? 5  
(b) Explain the various techniques used to control the electric drives. 5
3. (a) Draw the speed-torque characteristic of d.c. series motor and also write its expression. 5  
(b) What is chopper fed d.c. drive ? Explain with the help of a schematic diagram and waveforms. 5

4. A 220 V, d.c. shunt motor takes 50 A, when giving its rated output at 1500 rpm. Its total resistance is  $0.25 \Omega$ . Determine the resistance to be added in series with the motor to obtain the rated torque at (a) starting, (b) 1000 rpm. 10
5. A 230 V d.c. series motor used in lifts has a resistance of  $0.25 \Omega$ . It draws 40 A at a speed of 1500 rpm. Assume that the magnetization curve is a straight line between zero and 40 A, and the flux per pole at 60 A is 20% greater than at 40 A. Determine the resistance to be added in series with the motor for a speed of 3000 rpm at the current of 15 A. 10
6. Explain the working of Current Source Inverter (CSI) controlled 3-phase induction motor drive in the schematic, waveform and expressions. 10
7. (a) Explain the slip power recovery scheme in a.c. motor drive system. 5
- (b) Draw the speed-torque characteristic of 3-phase induction motor and explain its usefulness in drive application. 5
8. What is cycloconverter ? Explain its application in synchronous motor drive with schematic, waveform and expressions. 10

9. What is brushless d.c. motor ? How is its speed controlled with various methods ? 10

10. Write short notes on any *two* of the following :  $2 \times 5 = 10$

- (a) Solar and battery powered drives
  - (b) Four quadrant operation of d.c. drive
  - (c) Variable frequency control of synchronous motor
-