

**B.Tech. – VIEP – ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

00028

**December, 2015**

**BIEEE-018 : ADVANCED POWER ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any seven questions. All questions carry equal marks. Missing data, if any, may be suitably assumed. Use of calculator is permitted.*

---

---

1. Give the structure of an n-channel and a p-channel depletion-type MOSFET. Explain their operation and draw their transfer characteristic curve.  $4+4+2=10$
  
2. Explain the operation of a fully controlled bridge rectifier circuit with  $5+5=10$ 
  - (a) RL load
  - (b) RC load
  
3. What are the various modes of operation of an inverter ? Explain the operation of each mode with suitable diagram and waveforms.  $4+6=10$

4. Draw the circuit diagram and explain the working of a 3-phase bridge rectifier with necessary mathematical calculations and input-output waveforms. 10
  
5. What are the various areas of application of a current regulated voltage source inverter ? Explain in detail. 10
  
6. Differentiate between 3-phase square wave and a stepped wave inverter with the help of a necessary circuit diagram and mathematical calculations. 5+5=10
  
7. Explain the various types of static reactor compensation techniques based on thyristors, with advantages and disadvantages. 10
  
8. Explain the role of PWM current regulated VSI for static reactive VAR generation, with advantages and disadvantages. 10
  
9. Write short notes on any *two* of the following : 2×5=10
  - (a) Insulated Gate Bipolar Transistor (IGBT)
  - (b) Switched Mode Rectifier
  - (c) Shunt Reactive-power Compensators