

00696

No. of Printed Pages : 4

OIEE-001

B.Tech.
DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACCSVI

Term-End Examination

December, 2015

OIEE-001 : BASICS OF ELECTRICAL ENGINEERING

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five questions. All questions carry equal marks.

1. (a) Define and explain the following terms : 7
- (i) Resistivity
 - (ii) Conductivity
 - (iii) Potential Difference
 - (iv) Resistance Temperature Coefficient

- (b) For the given circuit shown in Figure 1, calculate R , if power dissipated in the circuit is 70 W when applied voltage is 20 V across the circuit.

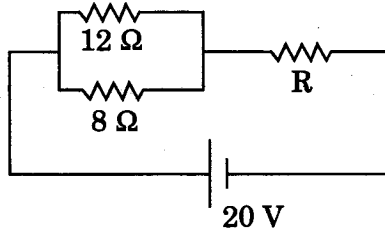


Figure 1

2. (a) By using Superposition Theorem, find the current in $R = 1\ \Omega$ resistor for the circuit shown in Figure 2.

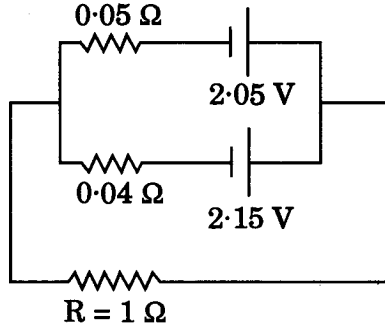


Figure 2

- (b) State and prove Thevenin's Theorem.
3. (a) Distinguish between primary and secondary cells.
- (b) Explain the constant current method of charging battery.

4. (a) Derive the expression for the force experienced by a current carrying conductor placed in a magnetic field. 7
- (b) What do you understand by magnetic circuit ? Explain the terms reluctance and magnetomotive force of a magnetic circuit. 7
5. (a) What do you understand by statically and dynamically induced emf ? Write down the difference between them with examples. 7
- (b) Prove that the energy stored in an inductor is $\frac{1}{2} LI^2$. 7
6. (a) An alternating current is represented by $i = 70.7 \sin 520t$. Determine the frequency, rms and average value of the current. 7
- (b) Define the following : 7
- (i) Active Power
 - (ii) Reactive Power
 - (iii) Apparent Power
 - (iv) Power Factor

7. (a) Explain resonance in parallel R-L-C circuits. 7
- (b) An R-L series circuit as shown in Figure 3 is connected across 240 V, 50 Hz, 1- ϕ a.c. supply. If the voltage drop R is 100 V, then find the voltage drop across the inductor L and also the value of L. 7

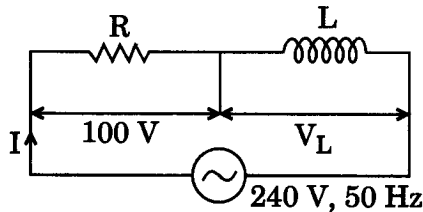


Figure 3

8. (a) Derive the relation between line current and phase current for a three-phase three-wire system. 7
- (b) What are the advantages of a three-phase system over a single phase system? 7