

**B.Tech. Civil (Construction Management) /  
B.Tech. Civil (Water Resources Engineering)**

00563 **Term-End Examination**  
**December, 2016**


**ET-202(B) : PRINCIPLES OF ELECTRICAL  
SCIENCES**

*Time : 3 hours*


*Maximum Marks : 70*

***Note :** Answer any **five** questions. Each question carries  
equal marks. Use of calculator is permitted.*

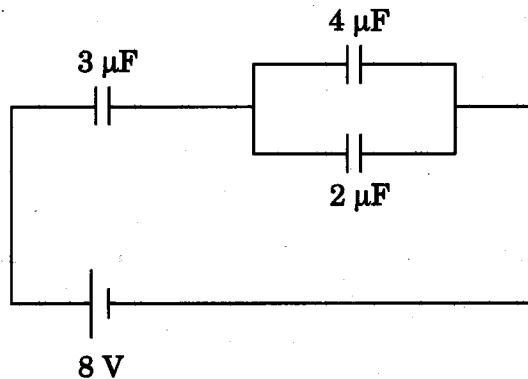1. (a) State and explain Maximum Power Transfer theorem and prove it. 7
- (b) Calculate the energy stored in the  $4\ \mu\text{F}$  capacitor and charge on the plates of the  $3\ \mu\text{F}$  capacitor. 7



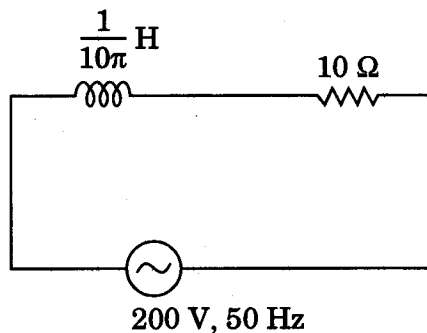2. (a) In the given figure,  $L = \frac{1}{10\pi}$  Henry,  $R = 10 \Omega$ .



Calculate :

7

- (i) Power factor of the a.c. circuit
- (ii) Voltage drop across the inductor
- (b) Regarding a system function, explain the following :
- (i) Forced response to an exponential input
- (ii) Frequency response
- (iii) Step response

7

3. (a) Give the construction and working of Autotransformers and Audio Frequency Transformers.

7

- (b) With the help of a neat and clean diagram, explain the constructional features of a direct current generator.

7

4. (a) Explain the speed – torque characteristics of shunt motors and also explain their speed control. 7
- (b) Discuss the constructional features and working of a three-phase induction motor. 7
5. (a) Explain the construction and working of a moving iron instrument. 7
- (b) Draw the voltage – current characteristics of a diode and explain its application in a full wave rectifier. 7
6. (a) Explain the transistor action of a Field Effect Transistor and give its V – I characteristics. 7
- (b) Discuss the working of a differential amplifier and explain the term CMRR. 7
7. (a) Explain various kinds of Flip-Flops used as digital building blocks. 7
- (b) What is a microprocessor ? Give an idea about its input-output ports, memory interface design and applications. 7
-

