

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2016

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS
DESIGN**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed and mentioned. Use of scientific calculators is permitted.

1. (a) For the current-mirror circuit shown in Figure 1, prove that the current ratio (I_2/I_1) is given as

$$\left(\frac{I_2}{I_1}\right) = \frac{\beta(\beta+1)}{\beta(\beta+1)+2}$$

5

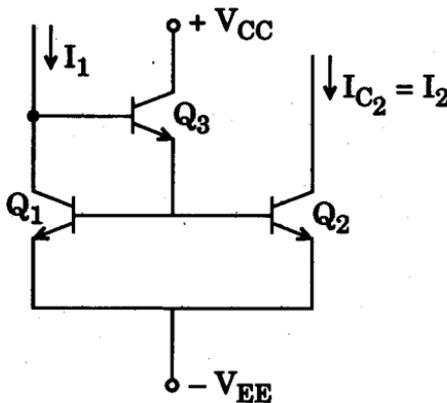


Figure 1

- (b) What are the reasons for using level-shifter in an IC op-amp ? Explain the operation of a level-shifter with the help of a neat diagram. 5
2. Draw the circuit diagram of a differential amplifier with active load. Explain its operation. What do you mean by complementary emitter-follower circuit employed in output stage ? Discuss it. 10
3. Explain the operation of a difference amplifier using three op-amps. Derive an expression for its output voltage and discuss how it can be used as an instrumentation amplifier. 10
4. Explain the use of current-to-voltage converter as a digital-to-analog converter. 10
5. (a) Find V_o for the circuit shown in Figure 2. 5

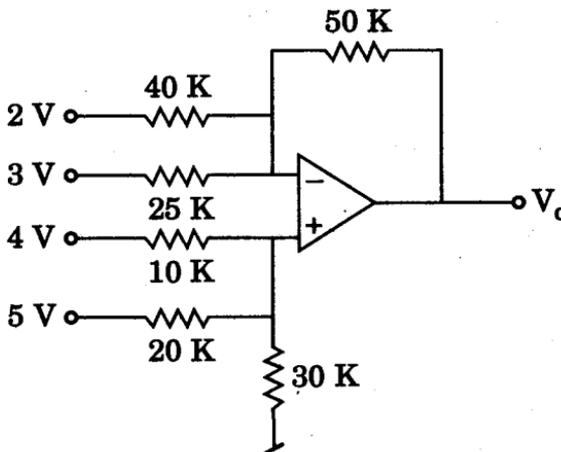


Figure 2

- (b) Explain the operation of a positive peak detector with the help of a neatly labelled circuit diagram. 5
6. Draw and explain the operation of an RC phase-shift oscillator and deduce the necessary condition and frequency of oscillation. 10
7. Explain the operation of an op-amp as a monostable multivibrator. Also derive an expression for the time-period of the output waveform. Under what conditions does the time-period become
 $T = 0.693 RC$? 10
8. Draw the circuit diagram of a second-order Sallen-key Band-pass filter. Derive an expression for its transfer function and calculate various filter parameters. 10
9. Explain the operation of V/F and F/V converters. 10
10. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) Analog Multipliers
 - (b) PLL as an AM Demodulator
 - (c) Monolithic Timers
-