

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2016

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks. Assume any missing data suitably. Use of scientific calculator is allowed.*

1. (a) For a given number $(1437)_{10}$, obtain its equivalent excess-3 code and gray code. 5
- (b) Simplify the given Boolean expression using Boolean algebra : 5
$$F = \bar{A}\bar{B}CD + \bar{A}BCD + AB\bar{C}D + ABC\bar{D}$$
2. (a) Design and implement a full adder using multiplexer. 5
- (b) Design a 3-bit priority encoder. 5
3. (a) Define the following terms : 5
 - (i) Excitation Table
 - (ii) State Table
- (b) Design a Mod-7 ripple up-counter. 5

4. (a) Simplify $F = \Sigma m(1, 3, 7, 10, 13) + d(0, 2, 4)$ using K-map. 5
- (b) Design and implement D flip-flop using JK flip-flop. 5
5. (a) Draw and explain the working of a TTL NAND gate. 5
- (b) Explain, how MOSFET acts as a switch. 5
6. (a) Differentiate between static and dynamic RAM. 5
- (b) Draw and explain the working of a static RAM cell. 5
7. (a) Differentiate between ROM, PLA and PAL. 5
- (b) Implement $y = 5x + 3$ using multiplexer, where x is a 3-bit number. 5
8. Simplify $F = \Sigma(0, 3, 5, 7, 13, 14, 15)$ using K-map and implement the simplified expression using Universal gates. 10
9. (a) Design a 4-bit binary-to-gray code converter using PROM. 5
- (b) Write notes on the following : 5
- (i) FLASH Memory
- (ii) EPROM
10. Design a Mod-8 synchronous up/down counter using JK flip-flop. 10
-