

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

**Term-End Examination
December, 2016**

BIEL-011 : LINEAR INTEGRATED CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, may be suitably assumed.*

1. Design an active load for an emitter-coupled pair (differential amplifier) and perform a detailed analysis to find its differential mode gain and the output resistance. 10

2. Obtain the frequency response of an open-loop op-amp and discuss about the methods of frequency compensation. 10

3. Define offset voltage. Explain a method to nullify offset voltage. 10

4. (a) Enlist the specification of a typical OP-AMP (741). 5
- (b) What are the limitations in a temperature compensated Zener-reference source? 5
5. (a) Design a low pass filter with a cut-off frequency of 1 kHz and with a pass band gain of 2. 5
- (b) Discuss the operation of a monostable multivibrator. 5
6. Explain the functions of all the basic building blocks of an op-amp. 10
7. (a) With neat sketch representations, explain the operation of positive peak follower. 7
- (b) State the advantages of sample and hold circuits. 3
8. (a) Mention the ideal characteristics of an operational amplifier. 5
- (b) State the causes for slew rate in an operational amplifier? How is it indicated? 5
9. Explain the triangle wave generator with a neat diagram and derive the expression of time period. 10

10. Write short notes on any *two* of the following :

$2 \times 5 = 10$

- (a) Phase Shift Oscillator
 - (b) Frequency Response of Non-compensated Op-amp
 - (c) Voltage-to-Current Converters
-