

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2016

BIEL-019 : POWER ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. Draw neat waveforms and circuit diagrams. Use of scientific calculator is allowed. Missing data, if any, may be suitably assumed.

-
1. Explain the two-transistor analogy of a thyristor. Explain any one of the turn-on methods. 10
 2. What is meant by commutation of SCR ? Draw the circuits and explain any two methods of forced commutation of thyristors. 10
 3. A full wave rectifier with centre tapped transformer, is feeding a resistive load of resistance R . Assuming that diode has zero forward resistance and infinite reverse resistance,
 - (a) find the expressions for V_{dc} , I_{dc} , V_{rms} , I_{rms} and efficiency.
 - (b) If the peak value of transformer secondary voltage from mid-point to each end is 100 V and $R = 5 \Omega$, find V_{dc} , I_{dc} , V_{rms} , I_{rms} and efficiency. 10

4. Draw and explain the wave shapes of supply voltage, output voltage, load current, current through SCR, current through freewheeling diode and voltage across SCR of a single-phase half wave controlled rectifier feeding R-L load. 10
5. Draw the circuit diagram of a single-phase dual converter and explain its working for both modes of operation. 10
6. What is McMurray full bridge 1- ϕ inverter ? Draw its diagram and discuss its operation. 10
7. (a) Draw and explain the characteristics of IGBT. 5
- (b) A parallel inverter has input d.c. voltage of 40 V. It is desired that the output voltage be 230 V, 50 Hz and peak load current 2 A. Design a parallel inverter. Choose the correct ratings of thyristor. 5
8. Why is forced commutation necessary for choppers ? Discuss the operation of an auxiliary commutated chopper. Draw the circuits showing the different modes of operation. 10

9. What is an a.c. regulator ? Give some of its applications. Draw a circuit diagram and explain the working of static on load tap changer for transformers.

10

10. Draw and explain the operation of speed control of a d.c. series motor by a single-phase full converter for the continuous motor current. Also draw the associated voltage and current waveforms.

10

