

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00519

Term-End Examination

December, 2017

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. Assume any missing data suitably. Use of scientific calculator is allowed.

1. (a) For a given number $(4246)_8$, obtain its equivalent excess-3 code and gray code. 5
- (b) Simplify the given Boolean expression using Boolean Algebra
$$F(x, y, z) = \pi_m(3, 5, 7).$$
 5
2. (a) Design and implement a half subtractor using universal gates. 5
- (b) Differentiate between decoder and demultiplexer. 5

3. (a) Explain SR flip-flop using truth table. Also write its drawbacks. 5
- (b) Design a Mod-5 ripple up counter. 5
4. (a) Reduce the following function using K-map technique : 5
 $f(A, B, C, D) = \pi(0, 3, 4, 7, 8, 10, 12, 14) + d(2, 6)$
- (b) Derive T flip-flop using JK flip-flop. 5
5. (a) Compare and contrast the features of TTL and CMOS logic families. 5
- (b) Explain the following terms : 5
- (i) Fan-in
- (ii) Tristate gates
6. (a) Write short notes on PROM and EPROM. 5
- (b) Explain the principle of operation of bipolar SRAM cell. 5
7. (a) Give the classification of semiconductor memories. 5
- (b) Implement the function with a MUX : 5
 $F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$
8. Using K-map method obtain the minimal SOP and POS expressions for the function
 $F(x, y, z, w) = \Sigma(1, 3, 4, 5, 6, 7, 9, 12, 13).$ 10

- 9. (a) Draw a circuit of 2×1 MUX and 1×2 De-MUX. 5**
- (b) Write notes on the following : 5**
- (i) PLA**
 - (ii) Flash Memory**
- 10. Draw a six-stage ring counter and explain its operation. 10**
-