

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

00989

December, 2017

BIEL-011 : LINEAR INTEGRATED CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Use of scientific calculator is permitted. Missing data, if any, may be suitably assumed.

1. Draw the voltage transfer characteristic curve of an op-amp. List the three open-loop op-amp configurations. 5+5=10

2. List the characteristics of an ideal op-amp. Also define the following terms : 7+3=10

CMRR, Slew Rate and SVRR

3. What are the two basic differential amplifier configurations ? Briefly compare and contrast these configurations. 5+5=10
4. Define a filter. How are they classified ? List the most commonly used filters. 3+3+4=10
5. What is the difference between a comparator and Schmitt trigger circuit ? List the important characteristics of a comparator circuit. 5+5=10
6. (a) What do you mean by the term Voltage Limiting ? Explain the process to obtain voltage limiting. 5
- (b) Draw a circuit for converting a square wave into a series of '+ve' pulses. 5
7. Why is emitter resistance (R_E) replaced by a constant current bias circuit in a differential amplifier ? What is the use of cascode configuration in an op-amp ? 5+5=10
8. How are analog voltages multiplied using a log-antilog amplifier ? Explain with the help of a neatly labelled circuit diagram. 10
9. Design a 50 Hz active notch filter. 10

10. Write short notes on any *two* of the following : *5+5=10*

- (a) Absolute Value Detectors
 - (b) Clippers and Clampers
 - (c) Level Translator
-